

NAVAL No. S400.
R.A.F. Form 619

ROYAL AIR FORCE.

JAMES R. WILLIAMS. 3aR.
set. Analytic

Notebook for use in Schools.

917993. W1. 7465. 500,000. 5/45. P. & T.

James R. Bellair (Class No. 1)
Northern Polytechnic
Halloway Rd.
1947

Cal. Analysis

Circuit Analysis




- 1. V_{rms} Sin. alt.
- 2. I_{rms} Sin. alt.

Vector Analysis



$\phi = \cos^{-1} \frac{R}{Z}$

Complex Numbers

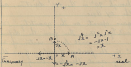

The position of the point A can be specified as $2.5 \angle 30^\circ$ or, as $5 + j8$
 Similarly the point C can be specified as $5 + j8$, or more simply $5 - j8$
 $D = -7 + j4$
 $E = -6 + j18$

VECTOR DIAGRAM

Let j be an operator such that when it operates on a vector OA it rotates 90° in the $+$ ve direction \rightarrow so that it becomes the vector OB .

$$\therefore j \cdot OA = OB$$

Taking j so defined, let it operate on the vector x , thus producing jx a vector of equal magnitude but rotated through 90° in the $+$ ve direction, and being along the oy axis.

Let j again operate on the quantity jx to give us the quantity j^2x . In from the defined properties of j , j^2x will be a vector of magnitude x rotated 90° in the positive direction from the position of the jx vector and therefore being on the Ox axis. It is therefore identical in magnitude & direction with a vector of $-x$.

$$\therefore j^2x = -x \quad j^2 \cdot ix = j \cdot (-i) = -1$$

$$\therefore j = \sqrt{-1}$$



The position of B can be expressed as $x + jy$

The vector OB can be represented graphically as shown or in its x & y components in the two perpendicular directions OX , OY . i.e. OB can say

that OB is the result of adding the quantities x & y vectorially. i.e. $OB = x + jy$ or $OB = x + jy$. Now the component of OB could also be written as $OB \cos \theta$ which is x and $OB \sin \theta$ which is y . i.e. $OB = r \cos \theta + r \sin \theta$
 $= r \cos \theta + j r \sin \theta = r(\cos \theta + j \sin \theta)$

Real
Imaginary } Quantities
Complex

ways of representing complex numbers such as the vector OB.

- (1) Graphically: - line drawn to represent it in Magnitude and direction
- (2) Cartesian form $x+iy$ is sum of real and imaginary component.
- (3) Polar form: $re^{i\theta}$ is specifying magnitude or Modulus r and angle or argument θ which it makes with the assumed reference angle line.

Conversion from Cartesian form to Polar. We must find the Modulus r and the argument θ .

From the diagram $r = \sqrt{x^2 + y^2}$ which could be $\sqrt{x^2 + (iy)^2}$


and $\theta = \tan^{-1} \frac{y}{x}$
NB. \tan^{-1} is a tangent whose angle is.

Ex. 1 Plot the following numbers on an Argand diagram and then put them in Polar form.

$$3+4i, \quad 3-4i, \quad 12+10i, \quad -2+3i, \quad -5-3i$$

Ex. 2 Change each of the following to the form $x+iy$
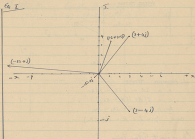
$$3/\sqrt{2}, \quad 2-2/\sqrt{2}, \quad 5/2/\sqrt{2}, \quad 6i/\sqrt{2}$$



Ex. 3 Change to the form $x+iy$

$$2/\sqrt{2}$$




$$y = 2 \sin 45^\circ \\ x = 2 \cos 45^\circ$$

$$6i/\sqrt{2}$$



$$y = 6 \sin 90^\circ \\ x = 6 \cos 90^\circ$$

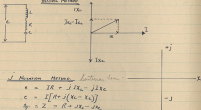Vector Method1. Phasor Method *Let us take*

$$a = IR + jIX_1 - jIX_2$$

$$c = I[R + j(X_1 - X_2)]$$

$$\frac{V}{I} = Z = R + j(X_1 - X_2)$$


$$\text{and } \bar{Z} = Z = R + j(X_1 - X_2)$$

Conversion to Polar Form

$$Z = \sqrt{R^2 + (X_1 - X_2)^2} \quad \angle \theta = \frac{X_1 - X_2}{R}$$

Addition of Complex Quantities - Rectangular Coordinates
x-y notation.
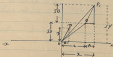
$$(A + jB) + (C + jD) = (A + C) + j(B + D)$$



$$\begin{aligned} OP &= (a + jb) \\ OQ &= (c + jd) \\ OR &= OP + OQ \\ OR &= (a + c) + j(b + d) \\ &= x + jy \\ &= (a + c) + j(b + d) \end{aligned}$$

Subtraction of Complex Quantities

$$(A + jB) - (C + jD) = (A - C) + j(B - D)$$

Multiplication -

$$\begin{aligned} (a + jb)(c + jd) &= ac + jad + jbc + j^2bd \\ &= ac + j(ad + bc) - bd \\ &= (ac - bd) + j(ad + bc) \end{aligned}$$

$$\therefore \angle \theta = \angle \phi \quad \angle \theta = \angle \phi \quad \angle \theta = \angle \phi$$

Multiplication: expressed in Rectangular coordinates of 1 notation form -

$$r_1 \angle \theta_1 \times r_2 \angle \theta_2 = r_1 r_2 \angle \theta_3$$

$$r_1 (\cos \theta_1 + j \sin \theta_1) \times r_2 (\cos \theta_2 + j \sin \theta_2)$$

$$r_1 r_2 = (\cos \theta_1 + j \sin \theta_1) (\cos \theta_2 + j \sin \theta_2)$$

$$r_1 r_2 = (\cos(\theta_1 + \theta_2) + j \sin(\theta_1 + \theta_2))$$

Division:

$$\frac{A + jB}{C + jD} = \frac{A + jB}{C + jD} \times \frac{C - jD}{C - jD} = \frac{A + jB}{C^2 + D^2} \times \frac{C - jD}{C - jD}$$

To complete the division we Rationalize the denominator we convert it from a complex form to a wholly real form. Note that to get the denominator into the desired form we can multiply it by anything we like provided we multiply the numerator & denominator by the same thing this does not alter the value of the fraction.

Note that $(a + b)(a - b) = a^2 - b^2$ and $a + b$ is called the conjugate of $a - b$, and $a - b$ called the conjugate of $a + b$.

$$\text{Similarly } (a + jB)(a - jB) = a^2 - (jB)^2 = a^2 - j^2 B^2 = a^2 + B^2$$

or Multiplying $a + jB$ by its conjugate $a - jB$ gives the wholly real result $a^2 + B^2$

$$\frac{A + jB}{C + jD} = \frac{A + jB}{C + jD} \times \frac{C - jD}{C - jD}$$

$$= \frac{(A + jB)(C - jD)}{C^2 + D^2} = \frac{AC - jAD - jBC + BD}{C^2 + D^2}$$

$$= \frac{AC + BD + j(BD - AD)}{C^2 + D^2}$$

$$= \frac{AC + BD}{C^2 + D^2} + j \frac{BD - AD}{C^2 + D^2}$$

$$= x + jy$$

Division Polar Notation

$$r_1 \angle \theta_1 \div r_2 \angle \theta_2 = \frac{r_1 \angle \theta_1}{r_2 \angle \theta_2} = \frac{r_1}{r_2} \angle (\theta_1 - \theta_2)$$

$$\text{Proof: } r_1 \angle \theta_1 = r_1 (\cos \theta_1 + j \sin \theta_1) = r_1 (\cos \theta_1 + j \sin \theta_1)$$

$$r_2 \angle \theta_2 = r_2 (\cos \theta_2 + j \sin \theta_2) = r_2 (\cos \theta_2 + j \sin \theta_2)$$

$$\therefore \frac{r_1 \angle \theta_1}{r_2 \angle \theta_2} = \frac{r_1 (\cos \theta_1 + j \sin \theta_1)}{r_2 (\cos \theta_2 + j \sin \theta_2)} = \frac{r_1}{r_2} \frac{(\cos \theta_1 + j \sin \theta_1)}{(\cos \theta_2 + j \sin \theta_2)}$$

$$\frac{r_1}{r_2} = \left[\frac{(\cos \theta_1 + j \sin \theta_1)(\cos \theta_2 - j \sin \theta_2)}{(\cos \theta_2 + j \sin \theta_2)(\cos \theta_2 - j \sin \theta_2)} \right]$$

$$= \frac{r_1}{r_2} \frac{(\cos \theta_1 \cos \theta_2 - j \sin \theta_1 \cos \theta_2 + j \sin \theta_1 \sin \theta_2 - \sin \theta_1 \sin \theta_2)}{(\cos^2 \theta_2 + \sin^2 \theta_2)}$$

$$= \frac{r_1}{r_2} \frac{(\cos \theta_1 \cos \theta_2 + \sin \theta_1 \sin \theta_2 + j(\sin \theta_1 \cos \theta_2 - \cos \theta_1 \sin \theta_2))}{1}$$

$$= \frac{r_1}{r_2} (\cos(\theta_1 - \theta_2) + j \sin(\theta_1 - \theta_2))$$

$$r_1 \angle \theta_1 \div r_2 \angle \theta_2 = \frac{r_1 \angle \theta_1}{r_2 \angle \theta_2} = \frac{r_1}{r_2} \angle (\theta_1 - \theta_2)$$

Proof: converting result to Polar form.

$$\text{Modulus} = \sqrt{\frac{r_1^2}{r_2^2}} = \sqrt{\cos^2(\theta_1 - \theta_2) + \sin^2(\theta_1 - \theta_2)} = \sqrt{\frac{r_1^2}{r_2^2} \times 1} = \frac{r_1}{r_2}$$

Argument to $\tan^{-1} \frac{Z(\omega) - R}{\omega L - \frac{1}{\omega C}}$ = $\tan^{-1} \frac{0}{0} = 0, 180, -90, 90$.

Polar Form is $\frac{V}{Z} \angle 0^\circ$.



$$I = \frac{E}{j\omega L + \frac{1}{j\omega C} + R} = \frac{E}{j\omega L + \frac{R - \frac{1}{\omega^2 C}}{R^2 + \omega^2 L^2}}$$

$$I = \frac{E}{R^2 + \omega^2 L^2} (j\omega L(R^2 + \omega^2 L^2) + R - \frac{1}{\omega^2 C})$$

at Resonance $I = E \angle (0 + j0)$

$$\therefore j\omega L(R^2 + \omega^2 L^2) - \frac{1}{\omega C} = 0$$

$$= \omega^2 L^2 + R^2 - \frac{1}{\omega^2 C^2} = 0$$

$$\omega^2 L^2 = \frac{1}{\omega^2 C^2} - R^2$$

$$\omega^2 = \frac{1}{LC} - \frac{R^2}{L^2}$$

To find the Impedance at Resonance (Complex Impedance)

$$Z_0 = \frac{E}{I_0} \angle \phi = \frac{E}{E} \angle 0 = \frac{R}{R^2 + \omega^2 L^2}$$

$$\therefore Z_0 = \frac{1}{\frac{1}{R} - \frac{R + \omega^2 L^2}{R}}$$

$$= \frac{R + (\frac{1}{LC} - \frac{R^2}{L^2})L^2}{R} = R + \frac{L}{R} - \frac{R^2}{R}$$

$$Z_0 = \frac{L}{R} = \frac{k}{CR}$$

Q for a component: Defined as the ratio of series reactance to series Resistance is $\frac{\omega L}{R}$ or $\frac{1}{\omega R C}$.

Q for a circuit: For any circuit Q is defined only at Resonance.

For a Series Ckt. $Q = \frac{\text{Total series Reactance of one kind}}{\text{Total series Resistance}}$

Both measured at Resonant frequency. $Q = \frac{\omega L}{R} = \frac{1}{\omega R C}$

Hence $Q = \frac{M \omega L \times \frac{1}{\omega C}}{R} = \frac{L}{CR}$

$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$

No. single number can be partly real and partly imaginary.

Hence $A + jB = 0$

$A = 0 \quad B = 0$

But that if $A + jB = C + jD$ (Eq. 1)

then $A + jB - C - jD = 0$

$(A-C) + j(B-D) = 0$

Applying above rule $A-C=0$ and $A=C$ (Eq. 2)

$(B-D)=0$ and $B=D$ (Eq. 3)

In any equation involving complex quantities the real part of one half of the equation will be equal to the half of the other equation. Similarly for the virtual part. Hence from the original complex equation two independent equations can be derived and that process is referred to as equating real and imaginary part.

From any bridge of the form -

The condition of balance is $Z_1 Z_3 = Z_2 Z_4$



Hence for Wheatstone bridge shown.

$(R_1 \frac{1}{\omega C}) R = M (\frac{1}{\omega C})$

$R R_1 - \frac{R^2}{\omega^2} = M^2 - \frac{M^2}{\omega^2}$



Equating Real and imaginary part $R R_1 - M^2 = R_2 - M^2$
and $-\frac{R^2}{\omega^2} = -\frac{M^2}{\omega^2} = \frac{R}{\omega C} = \frac{M}{\omega C}$ and $C = \frac{R}{M}$

* Series Element Impedance in Complex Notation



R



$+ j\omega L$



$-\frac{j}{\omega C} = + \frac{j}{\omega C} \quad \omega = -\omega$

Mutual Inductance



$E_2 = -j\omega M I_1$



$E_1 = -j\omega M I_2$

If the Resistance of a coil = R so that $I = \frac{E}{Z}$ the property of the coil can equally well be expressed by saying the coil has a conductance G equal to $\frac{1}{R}$ so that $I = E \times G$. Similarly if we have a series reactance X so that $I = \frac{E}{Z}$ we can express it properly by saying that it is a susceptance B equal

to find so that $I = E/Z$.

And if we have a set of Impedance Z so that $I = \frac{E}{Z}$ we can express the property of of the set by saying that it has an admittance Y equal to $\frac{1}{Z}$ so that $I = E \times Y$

In so far as R_x and Z are real and imaginary quantities, their Reciprocal would also be real and imaginary quantities.

Use of admittance-conductance

These are mainly of use in parallel circuit.

(29)



$$Y_{total} = G + B + j$$

Suppose $E =$ Voltage applied to set and $I_0 = I_Y$. The current therefore through the branches G, B, j

Then $I_G = E \times G$, $I_B = E \times B$, $I_Y = E \times j$ and

$$I_{total} = I_G + I_B + I_Y = E(G + B + j)$$

But $Y_{set} =$ Admittance of whole set

$$I_{total} = E \times Y_{set}$$

$$\text{Hence } I_{total} = E(G + B + j) = E Y_{set}$$

$$\therefore G + B + j = Y_{set}$$

$$Y_{set} = G + B + j. \text{ Now } Z = \frac{1}{Y} = \frac{1}{G + B + j}$$

Now Z is reciprocal ohms, a reactance of ω ohms has a G of $\frac{1}{\omega}$ Mhos $\frac{1}{\omega}$ Mhos

Reactance of $\frac{1}{\omega}$ ohms has a

susceptance of $\frac{1}{\omega}$ Mhos or 1 ohms



Series Resonance

$$\text{For set shown } i = \frac{E}{Z} = \frac{E}{R + j\omega L - \frac{1}{j\omega C}}$$

$$= \frac{E}{R + j(\omega L - \frac{1}{\omega C})}$$

Defining resonance as the condition which occurs when i is in phase with E , we see that resonance will occur when $\omega L = \frac{1}{\omega C}$. Because $i(R + j(\omega L - \frac{1}{\omega C})) = E$ and as E is a real quantity i must be wholly real to be in phase with E .

Putting $\omega L = \frac{1}{\omega C} = 0$ we have $\omega L = \frac{1}{\omega C}$ and $\omega^2 = \frac{1}{LC}$ and putting $(\omega L - \frac{1}{\omega C}) = 0$ in the original equation we have $i = \frac{E}{R}$ or $\frac{E}{R} = R$. That is impedance of set at Resonance = R .

Parallel Resonance



$$i = \frac{E}{R + j(\omega L - \frac{1}{\omega C})}$$


For resonance i and E in phase, the imaginary part of the RHS of the equation must be zero. That is $\omega L = \frac{1}{\omega C}$


whence $\omega^2 = \frac{1}{LC}$ and $i = \frac{E}{R}$. So that $\frac{E}{R}$ = impedance of set at Resonance = R .



$$\begin{aligned} * i &= \frac{E}{R + j(\omega L - \frac{1}{\omega C})} = \frac{E}{R + j(\omega L + \frac{1}{\omega C})} = \frac{E}{R + j(\omega L + \frac{1}{\omega C})} \\ &= \frac{E}{R + j(\omega L + \frac{1}{\omega C})} \end{aligned}$$




$$= \frac{E}{R + j(\omega L + \frac{1}{\omega C})} = \frac{E}{R + j(\omega L + \frac{1}{\omega C})}$$

Question

- 1) Show that for these two circuit  the maximum energy stored by the condenser is equal to the maximum energy stored by the coil, when the circuit is operating at the Resonant frequency. Show that it is approximately true for this circuit 

 
- 2) Show that when this circuit  is at Resonance there is a circulating current I_c which is equal to Q times the feed current I_f .

  - 3) Show that for both these circuit   the impedance of the whole circuit at resonance = Q times impedance of one reactive arm.

   - 4) The two coil shown are equivalent. Find an exact expression for R_p in terms of X_p & R_s .
 $X_p = X_s$
 $R_s = R_p$
 $X_s = X_p$
 $R_p = 0 \cdot R_s$

Answer

- 1) For the first two coil at resonance
 $\omega = \frac{1}{\sqrt{LC}} \Rightarrow L = \frac{1}{\omega^2 C} \Rightarrow \omega L = \frac{1}{\omega C} = \frac{I}{\omega C} \times C$
 But $\frac{I}{\omega C} = I \times X_c = E_c \Rightarrow \omega L = \frac{I}{\omega C} \times C = E_c \times C$
 $\Rightarrow \omega L = I_c \times C$

 - 2)  $I_f = \frac{E}{Z} = \frac{E}{R} \quad Q = \frac{\omega L}{R} \Rightarrow Q \times I_f = \frac{\omega L}{R} \times \frac{E}{R} \times R$
 $= E \times \omega L = I_c$

Effect of damping on a series circuit



If switch closed ($\omega = \omega_0$) $Q = Q_0$ (high)
 Show that with extra damping
 ($\omega = \omega_0$) $Q = Q_0 = Q_0 \left(\frac{R_0}{R+R_0} \right)$

$$Z \text{ with } \omega \text{ closed} = R + R_0 + j \left(\omega L - \frac{1}{\omega C} \right)$$

$$Q \text{ of the coil} = \frac{\omega L}{R+R_0}$$

$$Q_0 = \frac{\omega L}{R_0}$$

$$\text{Multiply } Q = \frac{\omega L}{R+R_0} \times R = \frac{\omega L R}{R(R+R_0)}$$

$$= Q_0 \left(\frac{R_0}{R+R_0} \right)$$



Parallel circuit

If with $\omega = \omega_0$ $Q = Q_0 = \frac{R_0}{R}$
 Show that $Q_1 = Q_0 \left(\frac{R_0}{R+R_0} \right) = Q_0 \left(\frac{R}{R+R_0} \right)$

$$\omega \text{ open } Q = Q_0 = \frac{R_0}{R}$$

$$\omega \text{ closed } Q = Q_1 = \frac{R_0 \times R}{R+R_0}$$


$$\text{From } \textcircled{1} \quad Q_0 = \frac{R_0}{R}$$

Substituting in $\textcircled{2}$

$$Q_1 = \frac{R_0 \times R}{R+R_0} = Q_0 \frac{R}{R+R_0}$$

But Q for circuit is defined at resonance, and at resonance R_0 the dynamic resistance of the coil
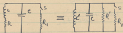
$$\text{Hence } Q_1 = Q_0 \left(\frac{R_0}{R+R_0} \right)$$



at $\textcircled{1}$

at $\textcircled{2}$

For at $\textcircled{1}$ $R_0 = \frac{1}{\omega^2 C^2}$
 Hence with $\omega = \omega_0$ $Q = Q_0$
 \therefore ... actual $Q = Q_1$

$$Q_1 = Q_0 \frac{R_0}{R+R_0}$$

at Resonance $R_0 = R'$ with $\omega = \omega_0$
 $\therefore R' = \frac{1}{\omega^2 C^2}$

For at $\textcircled{2}$ $Q_1 = Q_0 \frac{R}{R+R_0}$ just proved

$$\therefore Q = Q_0 \frac{R_0}{R+R_0}$$



Problem to find Z_1 , the impedance looking into L_1 ($\omega = \omega_0$, $Z_1 = \frac{E_1}{I_1}$)

$$-E_1 + I_1 \text{ j}\omega L_1 - j\omega M I_2 = 0$$

$$\text{or } E_1 = I_1 \text{ j}\omega L_1 - I_2 \text{ j}\omega M - E_2 \textcircled{1}$$

$$0 = I_2 (\text{j}\omega L_2 + I_1) - \text{j}\omega M I_1 - E_2 \textcircled{2}$$

$$\text{From } \textcircled{2} \quad I_2 = \frac{\text{j}\omega M I_1}{\text{j}\omega L_2 + I_1}$$

Substituting this value for I_1 in Eq. 0

$$E_1 = I_1 Z_{11} = \frac{j\omega M I_2}{j\omega L_1 + Z_{11}} \times j\omega L_1$$

$$E_1 = I_2 \left(j\omega L_1 + \frac{\omega^2 M^2}{j\omega L_1 + Z_{11}} \right)$$

$$\frac{E_1}{I_2} = Z_{12} = j\omega L_1 + \frac{\omega^2 M^2}{j\omega L_1 + Z_{11}}$$

