

MOD-

NAVAL No. S400.
R.A.F. Form 619.

ROYAL AIR FORCE.

~~EXPERIMENTS.~~ RADIO

Notebook for use in Schools.

~~MR. GIBBERTS.~~

~~MON AM 21~~

THURS - R 24 PM G

FRI - 25 PM II

James R. Williams
3 a R.

1947.

Experiment. 24. The measurement of choke input and
condenser input power filters.

~~Apparatus~~ Power Transformer. 240-0-240 V. 100 mA
1 Volt 2 Amp. C.T. 3 Amps
Valve rectifier to suit above
Two A.C.P. 100 Volt working condensers.
20 Henry smoothing choke
25 ohm ohm fixed resistor 3 watt.
250 ohm ohm variable resistor 2 watt.
Ammeter
Milliammeter 0-100 mA

~~Method~~ I. Connect the apparatus as shown in the
circuit diagram below taking care that the correct filament
winding is connected to the rectifier valves.


II. The purpose of the experiment is to compare the
effect of choke and condenser input filters on the
output voltage as the load current is varied. Taking
first the condenser input filter measure the voltage
with no load except for the load offered by the
voltage meter. Then connect the load resistor and
increase the current in steps of approximately 10 mA
until the maximum current of 100 mA is reached.
Note the output voltage at each increment.

ii. Disconnect the filter capacitor across the output valve and repeat the procedure.

iii. Plot the data to show the output voltage as a function of the load current.

iv. With no load on the supply, the voltage output is approximately the peak value of the 200 volt sine wave, or 300 v or 430 Volts. This is true with either condenser or choke input filter.

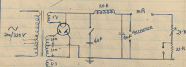v. Draw graphs from the above data, and deduce the reasons why the condenser input filter gives a higher voltage output at low drain and why the choke input filter produces a less variable characteristic.



See Appendix Book for Conclusions

Voltage Stabilizing


Non Stabilizer

If a voltage is applied across the cat. it is found that the voltage increases with a certain voltage is reached at which the gas comes. No current will flow through the ^{vacuum} until certain voltage is reached. Any slight rise in voltage would increase ionization the decreasing the resistance of the valve the increase in current flow is proportional to the decrease in resistance. Hence voltage across the tube will be constant. $V = IR$

Stabilizer



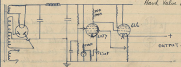Series of have arranged as shown in the diagram and enclosed in glass bulb with Helium and neon used. The striking voltage between each can be 20 Volts. Various voltages can be tapped off.



6U6 in series with HT. filament - load in the cathode varying or fluctuating - Fed to grid of 6U7. Screen voltage reasonably constant with 6U6 stabilizer. Cathode Voltage stabilizer by Non-Valve

iv. The series resistance of a fixed grid on increase of current plate there at the voltage plate would increase (V_g) voltage increase would only when at this stage to stability at the tube.



Function. Load current increases. Voltage at cathode of the tube decreases. The grid of the 6X4 goes +ve. The tube draws more current. Therefore the voltage rise across the grid of the tube is made more +ve.

Hard Valve Regulator

Any valve (hard) has a variable resistance across it because of variation of V_g .



R is necessary to act to control grid current.



Use tube instead of fixed potential - choose R, so that neon works at most efficient current (is about 10mA)

Tubes are more usually used because they are not so sensitive as triodes.

Pentode Regulator act.



Voltage stabilizer or better yet a valve.

Used in CRT power supplies. Does not control D.C. but smooths out ripple from D.C. (And back ripple cancelling) output ripple.



Resistors or Ballast Tube or Resistor



Iron wire in hydrogen envelope.

The tube is put in series with load current. If input changes, heating of the filament iron changes hence its resistance in filament. Voltage drop across valve changes and hence keeps the load voltage constant.

True Value Volt Meter

Advantages: Measures at high frequencies
 Over wide range of frequencies
 Has a very high input impedance
 Measures very small voltages
 Measures beyond of wave.
 i.e. Peak, R.M.S or Mean Value etc.

Disadvantages

Accuracy of calibration usually varies with change in valve characteristics H.T. Supply etc. Hence needs frequent re-calibration and is not usually so accurate as a D.C. M.C. Meter.
 May be subject to zero-point error.

Valve used as a detector

Grid-leak
 or Diode

To measure volt less than 10 volt except by amplification




Simple diode Volt Meter



The anode current produced is dependant on the applied voltage. The micro-ampmeter is calibrated directly in Volt. The calibration holds good for all frequency range. The advantage is that some Power is drawn from the source being measured.

CRT

Power Supply

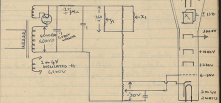

Time Base Graph: Charge and discharge of a condenser through Resistor.




On closing the switch condenser start charging. Rate of charge indicated on graph. Condenser will charge up until it acquires 67.26% of the applied voltage.

The charging voltage curve is exponential, but if the charging voltage is high a fairly straight line can be obtained, along which a time base can be operated.



Wave as Electronic Switch Non-Time Base

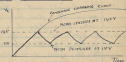

Condenser C charges up in the usual manner as shown. As the voltage increases to 100V the neon lamp strikes and hence discharges the condenser. Condenser voltage falls as it reaches 50 Volt the Neon discharges and as the condenser charges up again until it acquires 100V when the neon strikes and the cycle repeats itself. (Low Trill Time base is obtained)

Disadvantages of such Time Base.

- i. T.D. Small signal Amplification
- ii. Non Linear.
- iii. Fly back last too long. Saw toog.

The Variable Resistor R is used as a means of frequency control. Decrease would increase frequency. vice versa.

Condenser arrangement can also control frequency. With Variable Resistor Fine frequency control is obtained. With Condenser Coarse freq control.

To overcome non-linearity in the above C.R. combination. A Valve Diode or Pentode is used


instead of R. and the values are affected along the straight part of their characteristics \times as $\frac{1}{R}$ in the case.

Like to amplify μ wave from a means of applying greater current to the filament component giving rise to the characteristic.

The control is usually used, and fine frequency control is obtained by varying the Screen Voltage.



Integration Time Base

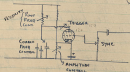

See Table T.B.



Velocity control frequency.
Trigger Fly back
Amp. control Amplitude.


With a control ratio 20:1. 9V bias on the grid corresponds to 180V anode potential. The condenser of the time base will charge until it potential reaches 180V. At the point ionisation takes place in the relay and the condenser discharges through it until it potential has fallen to below 20V when ionisation ceases and the discharge goes out. The range of voltage change across the condenser is 160V. To enable the trace of the beam to be accurately centred on the screen one of the plates is connected to a potentiometer across the H.T. supply (known as the X shift).

The advantages of the T.B. with respect to the screen is as follows:-

- (1) Better Amplitude
- (2) Better control
- (3) less more stable


Purcell's Time Base (Simple)

Negative going saw tooth

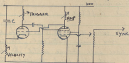



Grids conducting - voltage developed at the anode applied to the grid of the triode, as its cathode is at a high potential: the triode fails to conduct. Condenser C charges causing the cathode to fall in potential at a point when the triode conducts. As the triode conducts it anode falls consequently the grid of the pentode falls causing a rise at its anode. A larger positive bias is now applied to the grid of the triode, hence current will flow. C discharge rapidly, bring the cathode again at H.T., triode cut off. Grids conducting - operation repeat itself.

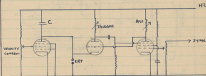As to wave form charging of C. Grid is employed, and C is made to charge over the straight part of its characteristics. The circuit now becomes:



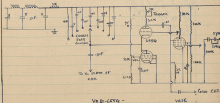Purcell Time Base as employed in Oscilloscope



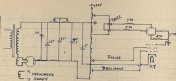

Power Supply - Universal CRO

Test Done - Universal CRO

Not working with
 for this model of CRO
 Try to use a different
 value of capacitor
 (100µF)

