

15 7 2 5	8 1 7 8 5
7 762	9 8.715.
15 - 15 - 100 f	90 $\frac{326 \times 10^3}{11} = 32600$
25 - 25 - 100 f	107
30 - 20 - 100 f	216
37 - 10 - 92 f	200
59 - 60 - 96-120 f	21 22
59 - 60 38 18	21 22
	21 22
18.6	21 22
=====	21 22
50000	21 22
10000	21 22

Conductors & Insulators.

Conductors are substances which readily permit the flow of electrons to take place under the influence of electrical forces & insulators are substances which under the same circumstances do not allow a flow of electrons.

Effects of Electric Currents.

1. Heating Effect. If wire carrying a current becomes heated (electric radiators, lamps).
2. Magnetic Effect. If wire carrying a current is exposed to magnetic field (motors & dynamos).
3. Chemical Effect. An electric current flowing through a liquid will decompose it (is not true) (Electroplating).

Unit of current (I) is the ampere (A).

The ampere is the practical standard for measuring current.

The International Ampere is the moving current which will deposits 0.001172 gms. of Ag. sec⁻¹ from a solution of its salts.

The Coulomb C. is the quantity of electricity passing per second when a current of 1A is the rate of flow i.e. $C = I t$

E.M.F. \Rightarrow P.D.

The E.M.F. required to cause a current to flow is measured in Volts (V)

The difference in Potential between different parts of a circuit is P.D. (V) & is measured in Volts also.

Resistance (R) is the opposition which the material forming the circuit offers the current; is measured in Ohms (Ω)

Ohm's Law

The current in a circuit depends upon the applied pressure & also upon the resistance.

Ohm's Law states that


$$I \propto E/R$$

$$\text{or } I = k E/R$$

By choosing suitable units let $k = 1$

$$\therefore I(\text{in amp}) = \frac{E}{R} \text{ in volt.}$$

Resistances in Series

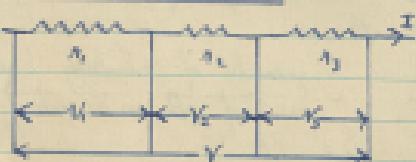

$$I = V/R_1 = V/R_2 = V/R_3 = V/R$$

$$\text{But } V = V_1 + V_2 + V_3 = I(R_1 + R_2 + R_3)$$

$$\therefore V/R = I$$

$$\therefore V = IR = I(R_1 + R_2 + R_3)$$

$$\therefore R = R_1 + R_2 + R_3$$

The equivalent resistance of a number in series is the sum of the separate resistances.

Resistances in Parallel.



$$I = V/R$$

$$I_1 = V/R_1$$

$$I_2 = V/R_2$$

$$I_3 = V/R_3$$

$$\therefore I = I_1 + I_2 + I_3$$

$$= V/R_1 + V/R_2 + V/R_3$$

$$\therefore \frac{1}{V} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$= \frac{1}{R}$$

$$\therefore R = \frac{1}{(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3})}$$

The reciprocal of the equivalent resistance is equal to the sum of the reciprocal of each separate resistance when in parallel.

Measure	C. G. S.	F. P. S.	Conversion
Length	Centimetre	Foot	1 ft = 30.48 cm
Mass	Gram	Pound	1 gm = 0.2957 gm.
Time	Second	Second	1 sec = 1 sec
Velocity	metres/sec ²	ft. sec ⁻²	
Acceleration due to gravity (g)	981 cm sec ⁻²	32 ft. sec ⁻²	
Tension	dynes	lb. wt.	1 lbwt = 444.8 newton
Work	Jab	Foot lb.	1 H.P. = 720 Jabs
Energy	Jab = 10 Jabs		= 32 ft. lb. sec ⁻²
Power	Watt = Jab/sec	H.P. = 550 ft/lb.sec	

$$1 \text{ H.P.} = 550 \text{ ft.lbs. sec}^{-1} = 550 \times 30.48 \times 0.29576 \text{ newton sec}^{-1}$$

$$= 550 \times 30.48 \times 0.29576 \times 981 \text{ newton sec}^{-1}$$

$$= 550 \times 30.48 \times 0.29576 \times 981 \text{ newton sec}^{-2}$$

$$= 7.46 \text{ watts}$$

Work, Energy & Power

Work is measured in Joules.

$$1 \text{ Joule} = 10^7 \text{ ergs.}$$

$$\text{Work done} = E.M.F. \times Q.$$

$$1 \text{ Joule} = 1 \text{ coul} \times 1 \text{ volt.}$$

$$1 \text{ Watt} = 1 \text{ Joule sec}^{-1}$$

$$= 1 V \times 1 coul. sec^{-1}$$

$$= 1 V \times 1 A.$$

$$\alpha W = E \times I.$$

$$W = I \times IR$$

$$= I^2 R$$

$$\alpha W = E \times \frac{E}{R}$$

$$= E^2 / R.$$

Specific Resistance.

$$R \propto l \quad (l = \text{length})$$

$$\text{So } R \propto \frac{l}{a} \quad (a = \text{area of cross-section})$$

$$\therefore R \propto \frac{l}{a}$$

$\alpha R = \rho \frac{l}{a}$ where ρ is constant for the particular material of the conductor called the Specific Resistance.

ρ is the measure of resistance between opposite faces of either a 1 cm² sided cube or 1 insided cube of the material.

Material	ρ in ohm	ρ in mho
Copper	1.61e-8	0.6322e-8
Iron	9.69	3.82
German Silver	20.0	11.8
Copper	19.0	19.2

Effect of heat on resistance

All metals (pure) increase in resistance with a rise in temperature.

Alloys, esp. "Resistance Materials" have a practically constant resistance.

Carbon & Insulators. decrease in resistance.

Within the normal temp. range (0 - 100°C)
the resistance of most conductors is given by
 $Rt = R_0(1 + \alpha t)$

Material	R_0 $^{\circ}\text{C.}$
Copper	0.0042
Iron	0.0062
German Silver	0.0084
Cureka	0.0000
Carbon	-0.05

Commercial Units.

1 Joule = 1 watt. for 1 sec.

1 Commercial unit of Electricity

or Board of Trade Unit = 1 kilo watt hour (K.W. hr.)

or B.O.T.U. = 1000 watt hours.

= 3,600,000 Joules.


Power	Energy
Watt.	1 Joule = 1 watt sec.
Kilo watt	Kilo Volt - hours
HP.	1 P. hor = 746 watt hrs.
	e.g. foot lb.

Internal Resistance of Cells.

Consider the internal resistance (r) as an additional resistance to an ideal cell.



Arrangement of Cells.

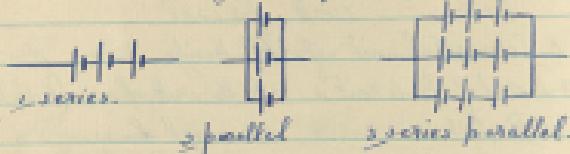

3. Total emf $\Sigma \mathcal{E}$ is the sum of separate emfs $\mathcal{E}_1 + \mathcal{E}_2 + \dots$.


Current is the same as for one

2. If I is A for one cell, cells should be identical; $\mathcal{E} = \frac{I}{R_1}, \frac{I}{R_2}, \dots$



I is the sum of each cell working I .

3. So a combination of the first two.

Potentiometer or Potential divider.

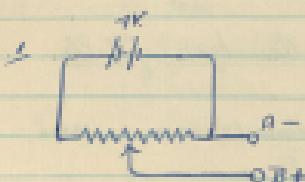

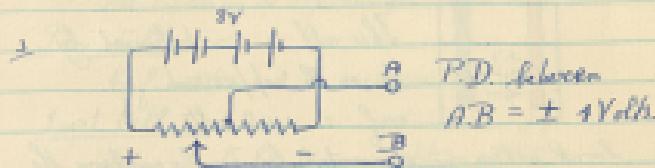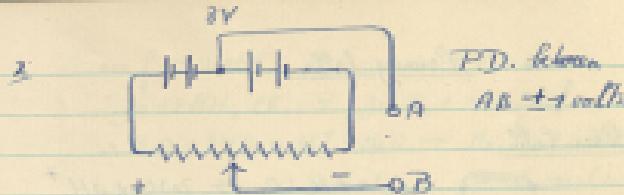Potential drop between
AB = 1 volt. \rightarrow 0.



The Current-carrying Capacity of cables etc.

The conductance of a conductor is the reciprocal of its resistance & is measured in mhos.

$$G = \frac{1}{R} \text{ or } G = \alpha$$

Safe rule for copper is to allow 1000A/m²

The size of a cable is governed by —


i) R loss (heat)

ii) IR voltage drop.

The current carrying capacity is the maximum current allowable under the specified condition without causing undue temperature or voltage drop.

Priamry Cells.


Voltai Cell

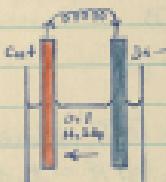

The cell is now polarised by
K or Cu sulphate.
emf = 1.08 volts.


Local action is prevented by amalgamating the
zinc.

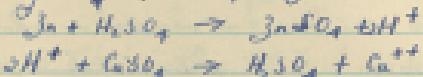Daniell Cell. is the above cell with a porous pot
containing CuSO_4 as depolariser.



The copper after losing its charge is plated onto
the copper rod.

Sébastopol Cell.

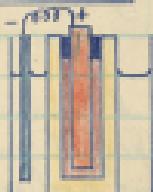

- Electrolyte, H_2SO_4 soln.
- +ve carbon rod.
- -ve zinc rod.
- pitch seal with gas vent.
- Depolariser, $\text{MnO}_2 + \text{C}$. dep.
- Porous pot.

$$\text{emf} = 1.46\text{V} \quad N = 1.0 \rightarrow 5.0 \text{ m.}$$



The carbon in the depolariser serves as a cathode.

Dry Cell.

$$\text{emf}, 1.5\text{V.} \quad N = 0.18 \rightarrow 0.9 \text{ m.}$$

Le Chatelier Cell

Same as Leclanche on addition of H_2O .

N.B. With solid depolarisers cell should only be
used intermittently.



Secondary Cells.



Lead-acid, Accumulator of Storage Cell

Both plates are coated initially with a mixture of
red lead + dilute H_2SO_4 & then are "formed" in charging.

Charging

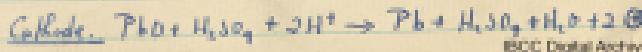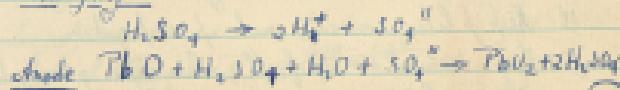

Discharging



Storage capacity is increased by increasing the active surface area of the plates.

Initial charge Standard voltage instructions.

Tests for completion of charge

i) Appearance of plates + a chocolate brown.
- white grey.

ii) Voltage - 0.5 to 0.7.

iii) Plates passing freely.

iv) Specific heat thermometer.

Care & Maintenance



- i) Do not over or undercharge at other stated rate.
- ii) Do not run nearly discharged batteries.
- iii) Do not stand the undischarged.
- iv) Keep plates covered, out of sunlight.
- v) Keep terminals + top of cell, clean, dry & greased.
- with vaseline.

Alkaline Cell or Nickel-Iron or Ni-Cd cell.

is robust, light + can stand discharged + can be overcharged or undercharged.

$$\text{E.m.f.} = 1.2\text{V.}$$

Charging Storage Cells

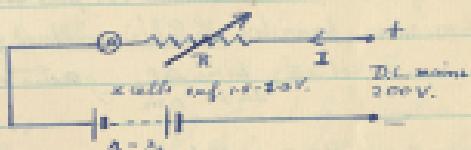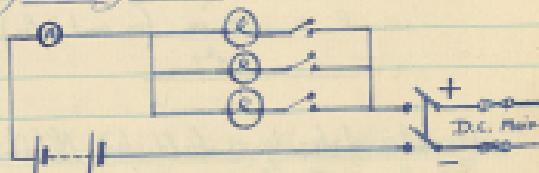

Since $R = \frac{V}{I}$ and we varying a variable resistor or lamps must be used to keep charging rate steady.

Example

$$\text{Initial Resistance R.} = \frac{200 - 150}{5} = 10\text{ ohm.}$$

$$\text{Final R.} = \frac{200 - 250}{5} = 25\text{ ohm.}$$

Magnetism

1. Unit of pole strength is that, when placed 1 cm. from a similar pole in vacuo is repelled with a force of 1 dyne.

Inverse Square Law

$$F \propto \frac{m_1 m_2}{r^2}$$

$$F = \frac{m_1 m_2}{r^2} \text{ (in unit poles)}$$

Magnetic Intensity or Field Strength (H) at a point is the force with which a unit test pole is repelled experiences, provided the field is unaffected by the presence of H = $\lim_{\Delta r \rightarrow 0} \frac{\Delta F}{\Delta r}$ gauss or dyne/pole.

$$\therefore H = \frac{m_1}{r^2}$$

Intensity of Magnetisation (I)

$$I = \frac{m}{r} = \frac{m}{2\pi r} = \frac{m}{a}$$

Magnetic Induction

Let B be 4π times of induction per unit pole (convention) in vacuo

i.e. at a distance r , from a pole, in vacuo.

$$\text{Total flux} (F) = \frac{m_1}{r^2} \text{ cm.}$$

$$\therefore B = \frac{4\pi m}{r^2}$$

$$= \frac{m}{r^2}$$

$$= H.$$

In vacuo the intensity is equal to the induction.

In a magnetizable medium

$$H \rightarrow$$



Since the force of the earth on magnet is notised by induction
then the force at T due to these forces
 $\Rightarrow 2IP/r^2$ where r is radius

Let I be intensity of dia. & if the dia. is very thin of magnetisation. The force = $2IP/r^2$ If per unit pole
 $\therefore m = IP$ where $m = 2I^2\pi r^2/a$ dyne/pole
 $= 4\pi I$ gauss

\therefore The total force = $H + 4\pi I$ gauss.

This is equal to the induction though

$$D = H + \sigma \pi I$$

The Magnetic Susceptibility of a medium, χ , is given by $I = \chi H$

The Permeability μ of a medium is given by $B = \mu H$.

$$\text{Since } B = H + \sigma \pi I$$

$$\mu = B/H = 1 + \sigma \pi I/H \\ = 1 + \sigma \pi \chi$$

In a medium of permeability μ ,

$$B = \frac{\mu}{\mu_0} H$$

$$= \mu H$$

$$H = \frac{m}{\mu \mu_0}$$

Gauss Law in



Let us imagine a closed surface drawn in a magnetic field.

Consider the flux across a small element of area, dA (as)

then D and H are normal induction across dA .

$$D \cos \theta dA$$

$$= \frac{m}{\mu_0} \times \cos \theta dA$$

Let $\theta_{\text{angle}} = \text{closed angle } \alpha$

$$D \cos \theta = m \cos \alpha$$

Total normal induction

$$= \int m \cos \alpha dA$$

$$= m \int dA$$

$$= m \times 4\pi$$

$$= 4\pi m$$

Gauss theorem states that the total normal induction of a closed surface is $+4\pi$ times the magnetic pole strength in the surface.

Total normal induction = flux.

The number of lines of induction from a unit magnetic pole.

Let a closed sphere of radius R have a single pole of strength m on unit poles at its centre.

By Gauss's theorem,

$$\text{The normal flux} = 4\pi m$$

Since all the flux is normal, the total flux from
1 unit pole = $4\pi m$ for lines
= 4π lines.

Hence the numerical value of the induction is equal
to the number of lines drawn through the considered area.

Magnetic Potential is the work done on one unit
polar pole in bringing it from infinity to the point
in question.

Let a dipole of m units be moved from a point
 a to $(r + dr)$ where $dr \ll r$ so that r intensity is constant.
Hence work done = force \times distance.

$$= -\frac{m}{r^2} \times dr.$$

V (Potential at the point)

$$= - \int_{\infty}^{r} \frac{m}{r^2} dr.$$

$$V = \frac{m}{r}$$

In a medium of permeability μ

$$V = \frac{m}{\mu r}$$


$$H = - \frac{\partial V}{\partial x} \quad \text{where } x \text{ is the distance
from the origin of
the force.}$$

Electro Magnetism.

A magnetic field surrounds a current flowing
in a conductor.



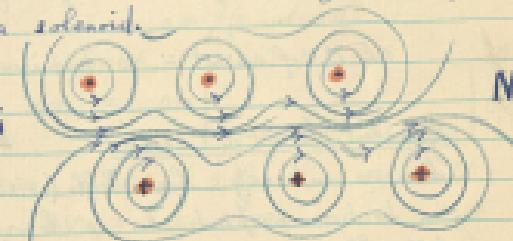The effect as in i_2 is increased by the no. of loops
as in a solenoid.



Electro Magnets

This is a coil of wire with a soft iron core usually
 $F = \mu_0 I N$ where I is the current
 & N the no. of turns.

The E.M.F. of current is that current when flowing
 in a coil of 1 cm, radius 1 cm the field it
 produces at the centre of its core is 1 gauss.
 i.e. in a loop 2 cm in radius the magnetic
 intensity at the centre = $\frac{2\pi M}{l}$ gauss
 = $2\pi i$ gauss
 when a current of i ampere is flowing.

$$1 \text{ E.M.F. of current} = 10 \text{ ampères.}$$

Equivalent Magnetic Shells

There are numerous thin shells (spherical) magnetized
 in a direction perpendicular to the surface of the
 shell. They are magnetized to an equivalent value
 so that produced by a certain current flowing through
 the periphery of the shell.

The strength, ϕ is the magnetic moment

per unit area.

$$\phi = \frac{I \times \pi}{a}$$

$$\therefore \frac{I t}{a} \quad \text{where } t \text{ is the thickness of the shell.}$$



Let a be the area of each
 face of element ABCD.
 \therefore the magnetization = I . a
 = a masy.

$$\text{The magnetic potential at } P \text{ due to ABCD} \\ = - \alpha m / (\rho + \tan \theta)$$

that due to CD

$$= - \alpha m / (\rho + \tan \theta)$$

where $\omega l = t$.

$$\Delta V_P = \frac{\alpha m}{\rho} \left[\frac{1}{\rho + \tan \theta} - \frac{1}{\rho + \tan \theta'} \right]$$

Let $\delta \rho \rightarrow 0$ where t & thus ρ is very small.

$$\Delta V_P = \frac{\alpha m \delta \rho}{\rho^2 + \tan^2 \theta}$$

$$= \alpha m \sin \theta / \rho^2$$

$$= I \cdot \pi t \cos^2 \theta / \rho^2$$

$$= \phi \cos \theta / \rho^2$$

Let $\omega_1 \cos \theta_1^2 = \omega_2$ where ω_2 is the solid angle subtended by shell at P.

$$\text{Hence } v_{P_1} = \phi \omega_2.$$

$\therefore v_P = \phi \omega$ where ω is the angle subtended by the shell at P.

Similarly on the other side of the shell

$$v_P = -\phi \omega.$$

The work done in carrying a unit +ve pole round a closed circuit.



Replace the circuit by an equivalent magnetic shell.

Consider P_1, P_2 close to opposite faces of the shell.

$$\therefore v_{P_1} = \phi \omega_1$$

$$\therefore v_{P_2} = -\phi \omega_2 \text{ where } \phi \text{ is the strength of the shell.}$$

Hence the work done in taking the pole from P_2 to P_1 is $\phi \omega_2 - (-\phi \omega_1)$

$$= \phi (\omega_1 + \omega_2)$$

where the shell is so big that P_1, P_2 coincide.

$$\omega_1 + \omega_2 = 4\pi r^2 \theta_1^2$$

$$= 4\pi r^2.$$

$$\therefore \text{The work done} = 4\pi \phi^2.$$

The magnetic field due to a circular current at a point on its axis.



$$v_P = i \omega \text{ where } \omega \text{ is the solid angle subtended by } AB \text{ at } P.$$

$$\omega = \Delta \times r^2 / x^2$$

$$= \Delta \sec(\text{bilateral}) / x^2$$

$$= 2\pi r^2 (1 - \cos \theta) / x^2$$

$$= 2\pi (1 - \cos \theta)$$

$$= 2\pi (1 - x/(r^2 + x^2)^{1/2})$$


The magnetic intensity at P

$$= \frac{dV}{dx} = 2\pi i r^2 / (r^2 + x^2)^{1/2}$$

Magnetism at O is found by putting $x=0$
 $\therefore H = \frac{2\pi i}{R^2}$.

The magnetic field due to a linear current.

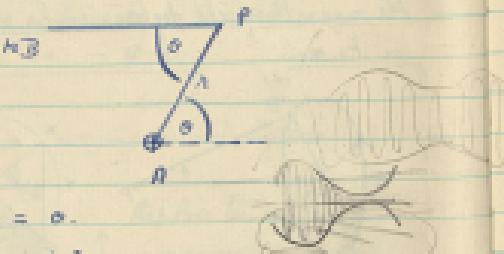Let P be a point, r distant from an infinite wire carrying current i . Let the return wire be at infinity.



$$\oint J_dS \cdot \vec{v} = 0.$$

$$w = \omega a.$$

$$\therefore v = \omega a.$$

$$\therefore H_p = -\frac{\partial \psi}{\partial x} \hat{x} \hat{a}_n$$

$$= -\sigma i \hat{x} \hat{a}_n$$

Magnetic field inside a long, straight solenoid.

Consider a solenoid having t turns per unit length
 i total current.

Then the circuit can be replaced by a magnetic shell.



$$P = i \cdot \hat{n} \quad \text{Intensity of magnetization per unit area.}$$

$$\therefore \text{The magnetic moment} I \\ = i \times \pi a^2.$$

$$\text{Let the thickness of the shell} = Va$$

$$\therefore \text{Pole strength} = \frac{M}{V} \times a^2 \\ = m/k \\ = \pi V a^2 i.$$

Let σ be the surface density of distribution of magnetism on the faces of the shells.

$$\text{Then } \theta = \pi i.$$

(consider P at the ends of the solenoid.)


$$H_p = +\pi \sigma \quad (\text{Gauss's theorem}) \\ = +\pi n i.$$

On between two shells to apply the law.

If P is in a shell, then shell must be split.


$$H_p = +\pi i \frac{T}{l}$$

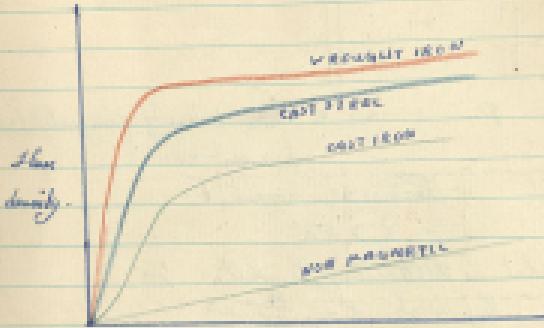where T is the total number of turns + l the length of the solenoid.



Magnetizing force.

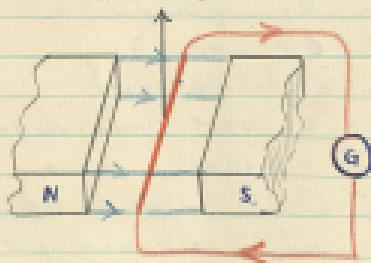Action of a moving conductor in a magnetic field



Change of flux linkages cause an emf to be produced in the conductor. The direction of which is given by Fleming Right-Hand Rule.

$E \propto \frac{d\Phi}{dt}$

This is the dynamic effect.

Action of a current in a magnetic field



By interaction of the magnetic field of the conductor & the initial field, the conductor moves the direction being given by Fleming left hand rule.

This is the motor effect.

Equations of the Dynamic Circuit

Consider a Toroid with a core of permeability μ_0 , mean radius r_{mean} , T turns & i current of current flowing through it.

$$H = \frac{2\pi i T}{2\pi r}$$

$$\text{but } B = \mu H$$

$$B = 4\pi \times 10^{-7} \frac{A}{m^2}$$

$$\text{but } \oint = Ba$$


$$= 4\pi \times 10^{-7} A^2 / 2\pi R$$

$$= \frac{A^2}{R^2}$$

$$2\pi R / \mu_0$$

\therefore Magnetic force / Resistance

Hysteresis Loop

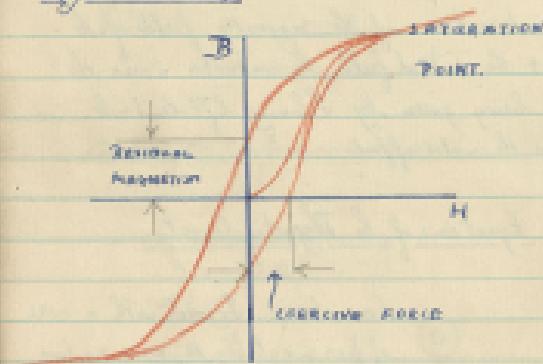

The demagnetization of iron consists of applying a slowly decreasing magnetic field by DC with a variable resistance in series.

Energy in a Magnetic Field

Consider a loop of area a in a B field.

In dt time a dB/dt lines of induction are set up

\therefore there are $nA dB$ flux linkages changing.

\therefore the heat in $f = nA \frac{dB}{dt} dt$ sec of potential

\therefore the current against this is i

\therefore the magnetic energy = $i dt \frac{dB}{dt} B^2/2 \pi$

$$\text{now } H = \frac{B}{\mu_0 i}$$

$$\therefore \mu_0 i = BH/4\pi$$

$$\therefore \text{Energy} = i dt \frac{\mu_0 A B^2}{4\pi} dt$$

$$= \frac{1}{4\pi} \mu_0 A B^2 \text{ ergs.}$$

$\mu_0 A$ is the volume of the field (or iron)

$$\therefore \text{the energy} = \frac{1}{4\pi} \int H dB \text{ ergs / unit vol.}$$

$$= \frac{1}{4\pi} \int \frac{B}{\mu_0 i} dB$$

$$= \frac{1}{4\pi} \int B^2 d\frac{B}{i}$$

$$= \frac{B^2}{8\pi \mu_0 i \text{ ergs / sec.}}$$

$$\text{or } \frac{10^{-12}}{8\pi \mu_0 i} \text{ ergs / sec.}$$

\therefore grid or mode loads. In reducing gear the grid circuit is usually biased & in series with the main circuit.

Magnetic field in a Solenoid

Consider a unit ~~in~~ pole carried once round the magnetic circuit.

The work done by the current in reducing

$$\text{The field} = 2\pi \times 4 \text{ ergs}$$

law of conservation of energy \rightarrow This is not due but the final effect is the same. (with diagram)

law of charge changes

$$= \frac{d\Phi}{dt}$$

: the flux change $= \frac{d\Phi}{dt}$ where t is the time

$$\therefore \text{the vol. day} = \frac{d\Phi}{dt} \times t$$

$$= 4\pi n i \text{ ergs}$$

$$R_{\text{ext}} = 2\pi R N$$

$$\text{length } H = \frac{2\pi R N}{R}$$

$$\text{but } l = R$$

$$\therefore H = \frac{4\pi R N}{l} \text{ ergs.}$$

It solenoid is part of an infinite solenoid so that this applies to the centre of a solenoid but not the ends.

Slowly decreasing magnetic field by i_{dc} with a variable resistance in series

current \rightarrow which was rising is reduced

The fall of I_a allows the field of R_c to partly collapse in change the direction of current. It reverses the direction of induced current in R_c & the grid becomes +ve. The +ve grid makes I_a rise again, the field, and I_a goes to the initial value which makes the grid negative repeats etc.


Each reversal of the field back adds a little to the oscillatory current in R_c until $I_a^2 R_c$ & other losses prevent further growth. When the oscillatory current has reached its max. value it will continue to fluctuate long as the valve is in operation. The frequency of the current is governed by $2\pi R_c$ & if these are adjustable it may be controlled desired. An amount of power, about but not quite equal to the amount of power available as feed back may be drawn from the circuit for external use. It neither lost from the production of oscillation point of view, unless the load circuit is connected in the grid or anode leads. In receiving gear the grid circuit is usually biased & in transmitting, the anode circuit.

If grid current is permitted to flow (i.e. if grid is operated at zero mean potential)

Will damp the circuit i.e. To prevent the bias is applied to triode by means of a battery or by means of self biasing action of a "leaky" grid condenser.

Self biasing by "leaky" condenser

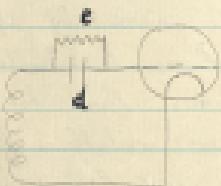When an oscillating voltage is applied between grid & cathode of a triode it flows during each one cycle. The leakage is deliberately provided to provide self biasing.




The zero potential attracts electrons from the cathode to the grid & these rush into & charge it in their efforts to return to the cathode. The leakage is such that a P.D. between its plates is set up. The plate connected to the grid is -ve. This, however, makes the grid -ve in turn. It. In the absence of load a further application of zero potential (i.e. more than half cycles) will result in a "spiking up" the charge in it & increasing the bias until it equals the peak value of the input (i.e. signal) (the value θ_{max})

The load R_L allows the charge to leak slowly away. The rate of leakage is adjusted to maintain the bias value of bias slightly less than the peak value of the zero half cycles so that end-to-end "overcharge" does not happen.


The bias is automatically adjusted to suit the conditions under which the valve is operating (i.e. if the amplitude of the oscillation increases the bias also changes).

Amplifier circuit

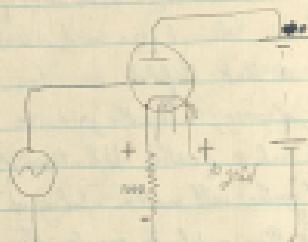

In A.F. unity.

Oscillator in transmitter

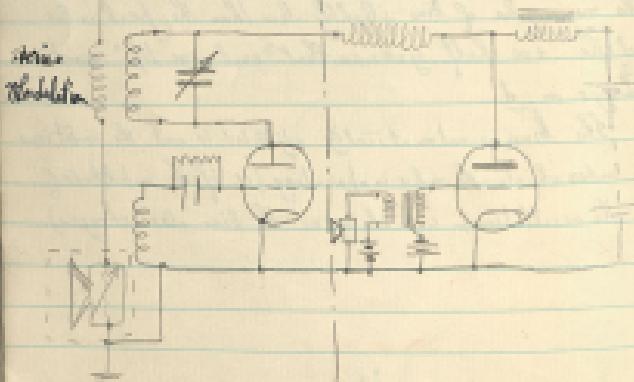

2 tubes will be controlled transmitter
(A.C. oscillator).


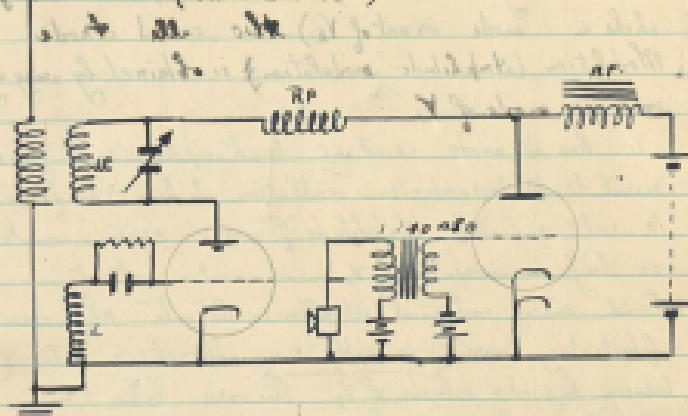


Fig. 2

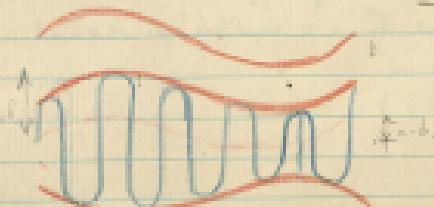

The circuit is of a practical transmitter using unmodulated (A.f.) volts & varying oscillation amplitude as described above if choke is made in out of V_2) Also called anode. Modulation (amplitude modulation) is obtained by varying volts on anode of V_2 .

V_2 has its anode circuit ac. back coupled to its grid circuit to produce continuous oscillation which is transferred to anode & radiated. Amplitude of carrier remains constant so long as current in V_2 anode circuit is constant. Small carrier induced vibrations on the "milk" solid mass of insulating support is supplied an alternating P.D. between C grid & cathode of V_2 . This varies V_2 's anode alternating voltage appears across the A.f. choke.

When the alternating P.D. across A.f. choke is in a. m. mode and it adds to the H.T. volts. & amplitude of oscillations so is increased. Conversely when alternating P.D. is -ve at m. mode and of A.f. choke it subtracts from supply volts & the a.c. amplitude is decreased.

The curve in fig. 2 is a "carrier wave" of fundamental of determined by a.c. constants & amplitude of H.T. & choke(V).


This const. wave fig. 2 is the wave effect of V_2 . Hence

is called the amplitude & angle of modulated waves due to speech or music.

The third form is - variation of carrier amplitude. This is done when modulated if the wave amplitude is not too big in amplitude the amplifier often follows an ideal a-b-c-a-b

It can not be realized in 2 stage circuit (transistor there). They are - using a. c. rectifier in series; the wave has to be differentiated. The carrier has to be converted into a steady voltage & a. c. component. Since the f. between 200-500 & working is a 10 kHz signal.

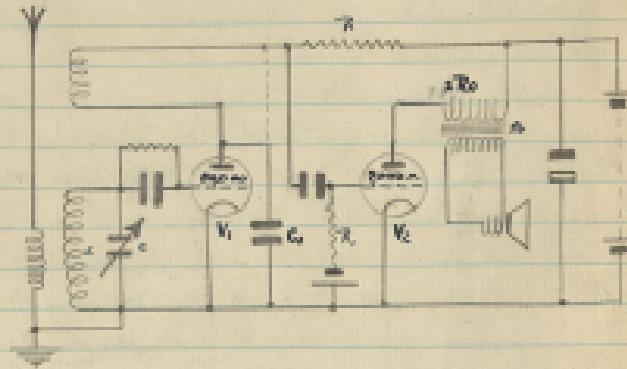The 10th of oscillation amplitude & frequency will be used. The first wave does not affect modulation. When the wave amplitude exceeds its own the amplitude will be limited.



$$n = \sqrt{2R_L / 3k T_{diode}}$$


2. Value resistor ($R = V - i$)

Signal, a small induced modulating current in the cathode varies in amplitude as does the modulation. The signal amplified by β of A.C. (subject to early grid damping) is applied between grid & cathode of 2nd valve. The bias derived by the early grid and over all may be supplied by modulation (i.e. the new value of I_C will follow modulation). Both R_f & A_f are present in anode circuit of V_2 & after a portion of the A_f has been used to provide feedback the R_f is disposed of. Last C_o . The A_f current develops a.f. voltage across R_f . R_f is in parallel

with R_L , so the load of V_2 is between grid & anode of V_2 so V_2 amplifier with load R_f across it provides conduction. Large current which is, finally passed for the operation of a.c. speaker.

Voltage control of generation.
Thermal Control

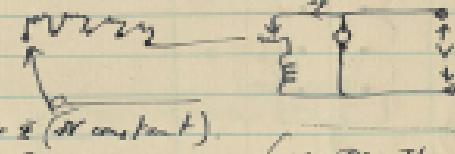
g. Varicore variable, usually about type.




$$V = RI, If.$$

b. Carbon thermal or Peltier.

Thermistor

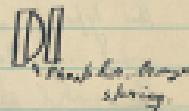

Automatic Voltage Control

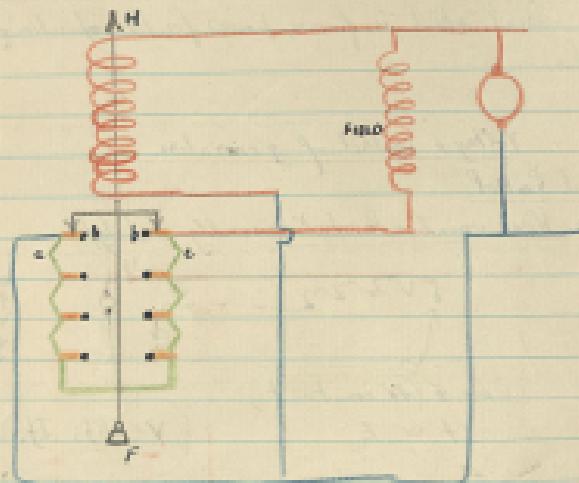


Carbon Pile Automatic Voltage regulators.


This type is simple & requires no attention. Field current can be controlled over a wide range.

The control element is connected across the generator terminals 'H' & 'F' which works by carbon stacks of carbon plates. The carbon plates which work about their ends have silver inserts b.d at the front & high resistance appears at the back o.e.

Forward movement of the control lever makes the slides forward bringing the slides contacts progressively into contact. Until the resistance of the slide is practically reduced to zero & reverse movement makes the slides backwards progressively separating the contacts & increasing the resistance. The two slide resistors connected in series or parallel are in series with the field circuit to be controlled. They will keep the generator voltage constant all in $\pm 2\%$.

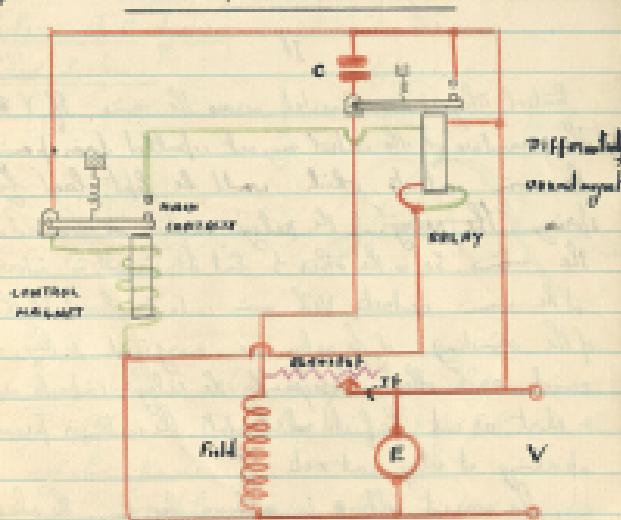

Control Relay delay regulation.

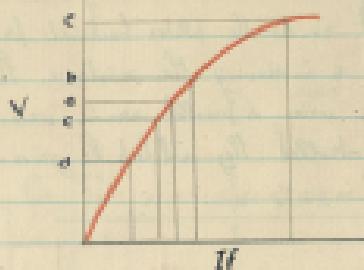


Control Relays are connected across the main. If V increases the armature of the control magnet repelled down opening the main contacts, which would be lifted apart by the spring. The relay & the relay winding is connected over the main. So is the other & but its circuit is interrupted at the main contacts. With main contacts closed both halves of the winding of the relay are energized & they, magnetically, pull each other. Consequently the relay contacts are closed & short circuit the field solenoid. The induced current opposing it relay contacts.

The control voltage is reduced by a rheostat's at 50% before main at Δ . If V falls to 6 .

The main contacts close, the relay is demagnetized & relay contacts close, shorting the solenoid. If V rises quickly & V would rise to 2 . However when V is raised the main contacts open & the solenoid is unshorted & V tends to 2 . The whole process repeats on so that V vibrates between $2\% & 2$. The vibration is extremely quick & V is constant to $\pm 0.5\%$.

Polyphase A.C. Systems

2 Phase System.

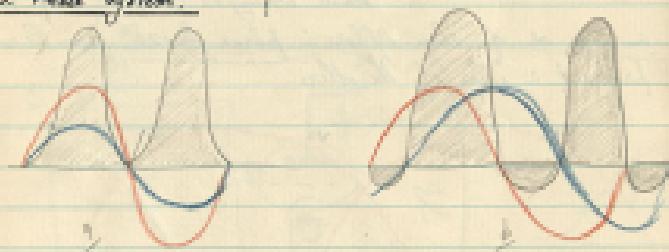

In a single phase system, the power absorbed varies as in a^2 . If current & voltage are out of phase a loss some negative power &


By using polyphase systems the periods of negative power can be eliminated & greater ratio of power obtained

If the 3 phase rotors have the advantage that the separate working circuits are simpler than in single phase circuits.

Three Phase Alternator.



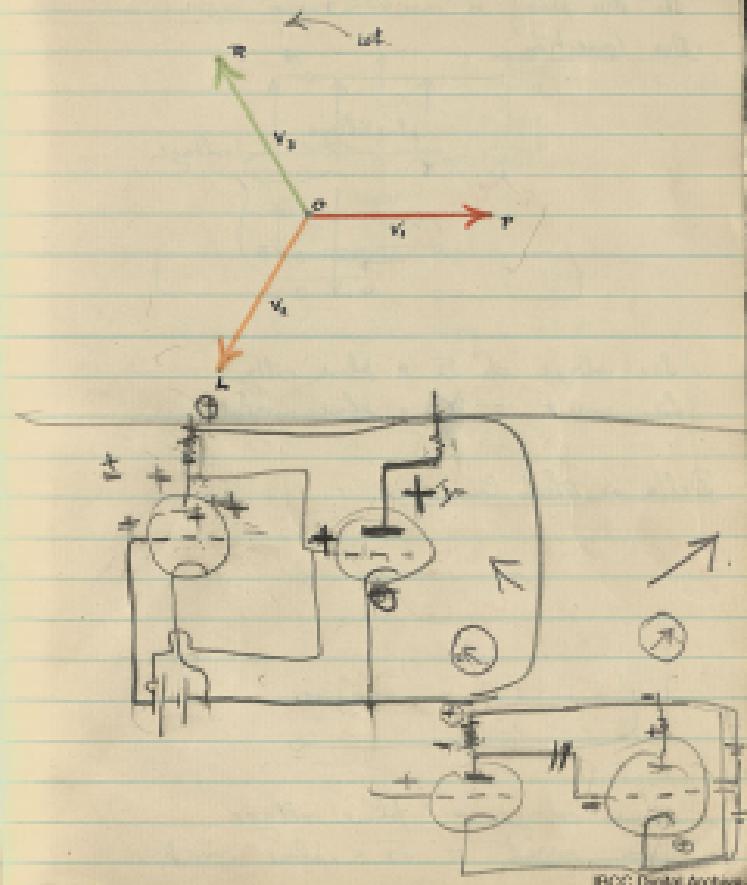This type has three distinct windings on its rotor, the ends produce equal alternating voltage in each of the windings. Rotating arms arranged that the emf produced in any one of them lags in phase by 120° from that produced in either of the others.



The three phases are connected in Y or Star connection.


Star connection



Line voltage = $\sqrt{3} \times$ phase voltage.

Line current = $\sqrt{3} \times$ phase current.

Three Phase wye system

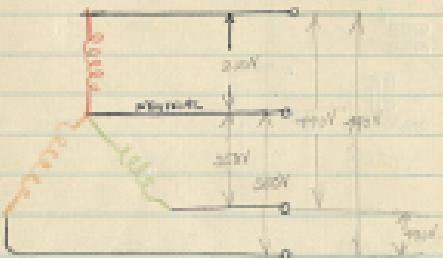


If voltage between two wires is $220V$, then
for one wire, voltage V between any two neutral
is $220/\sqrt{3} = 127V$.

Delta or Mesh connection




Line voltage = phase voltage


Line current = phase current.

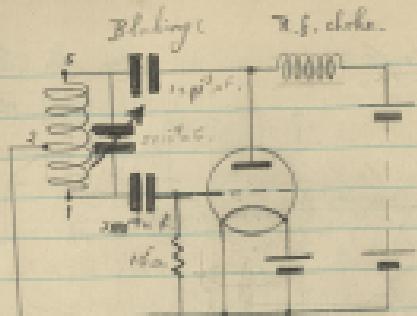


Hartley Oscillator

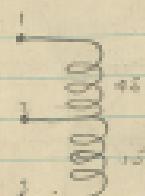

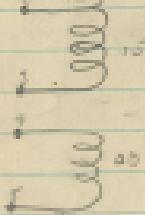Same as for what is
stated - i.e., 63, 100 u



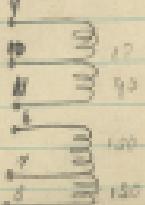For the development - Hartley
oscillator using a 100 u grid leak
circuit, the rate of change of the
current in the grid leak is very
slow. If the frequency is



With change of f_{ac} is large
 C is varied. Thus f_{ac} of L
against C .

Method of "squeezing"


Induced from anode to grid is called common
A.C. circuit - the blocking capacitor will
prevent L from shorting to cathode. The P.F.
inductor prevents the low voltage of the A.C. supply
from entering the valve as oscillations.

The L is under-tuned (i.e. voltage is low) so that it may
be just between grid & cathode without exciting the two
anodes.


The grid condenser & leak provide anti-resonance.
 L is also rather high in value to deliberately
cause "squeezing".



Conversion of A.C. to D.C.



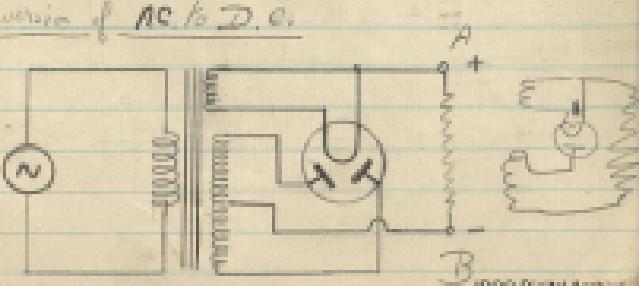


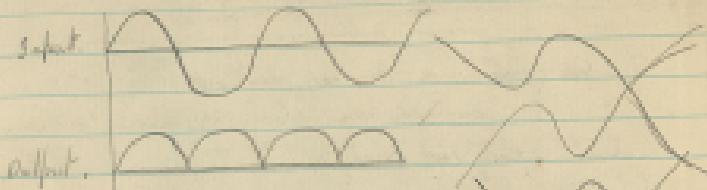Comparison of Full & Half Wave Rectification



Full wave rectification

involves 2 diodes (not suitable for a rectifier circuit by itself)

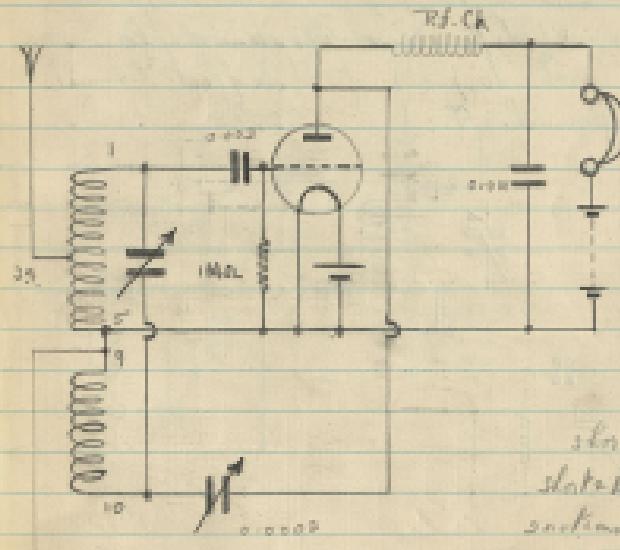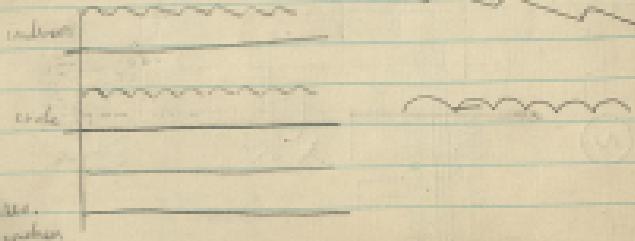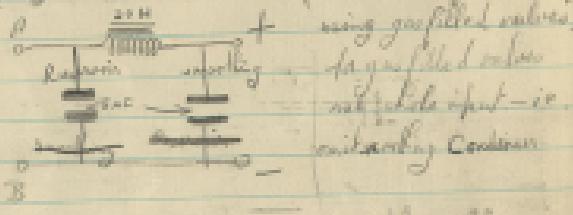

short 1000
stated by 8
continued

Sept 21-2. The gridely was made up with simple series modulation.


Received a commercial set for 1 MHz for a 200 m.

Sept 22. Received 2100 volt delecator with vacuum ray
modified slightly circuit - right side valve - note it is
a unidirectional power oscillator ~~one~~ point.

22a. Plate effect of grid bias to L7 +ve.

22b. Rf bypass to plate instead of filter.

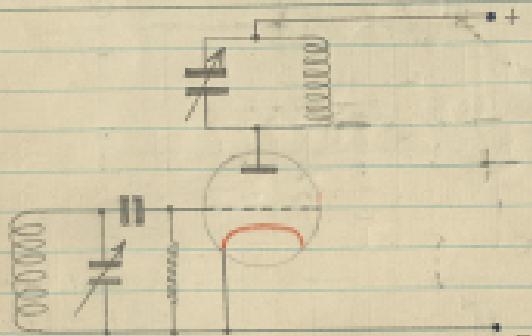
22c. Grid bias to plate & effect of small
C in series with AE.



T.P.T.G. Oscillator.

the function by virtue of the internal capacitance
of the valve (ie. C_{av}) providing feed-back.

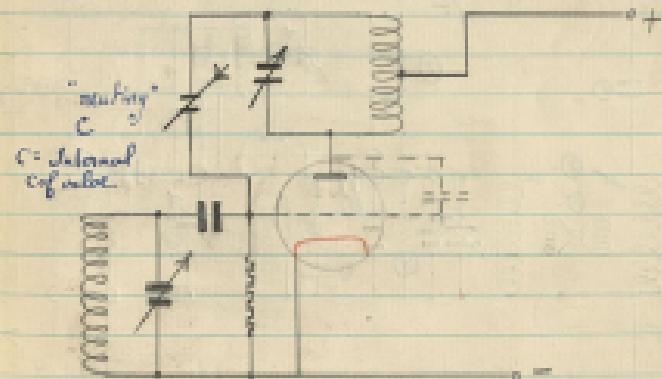It is essential that the anode voltage changes
in a regular direction (series) at the same instant
the grid changes in a positive sense (or 180° out
of phase with E_g) so that feed-back will take
place in the correct sense. The anode circuit
must be tuned to the same f. as the grid circuit.




Tuned Diode circuit showing neutralizing
(sealing).


Extract Philips Tech Journal Vol. 2 No. 6.

The figure circuit consists of a no. of parallel rods set up in a plane, which are coupled by the electrostatic field with each other & with the dipole. Each is coupled to the lines either a receiver. The length of dipoles & their mutual distances are determined experimentally so that max amplification is obtained in the direction in which the rods are situated no where else. The sketch gives an example for 3 dipole.

The action consists briefly of this. Let L_1 & C_1 from the most distant dipole induce such tensions in the various rods that the currents carried thereby & electrode connected to the receiver are added. If a reflection and so also introduced such as is indicated on the figure one obtains in result that the resultant signal which reaches the receiver has an amplitude greater than by a factor of 2.6 than if a single dipole were used.

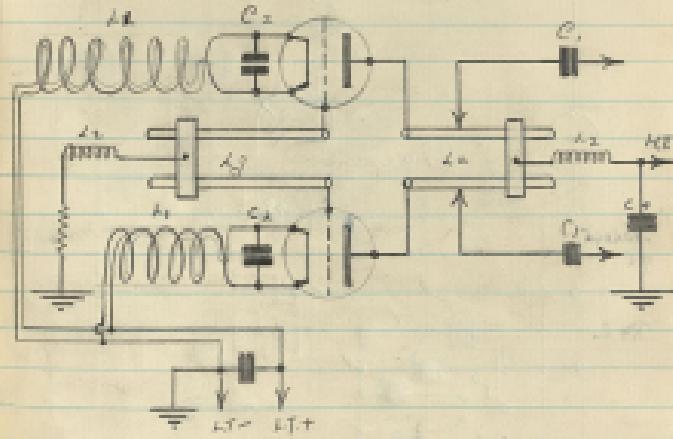


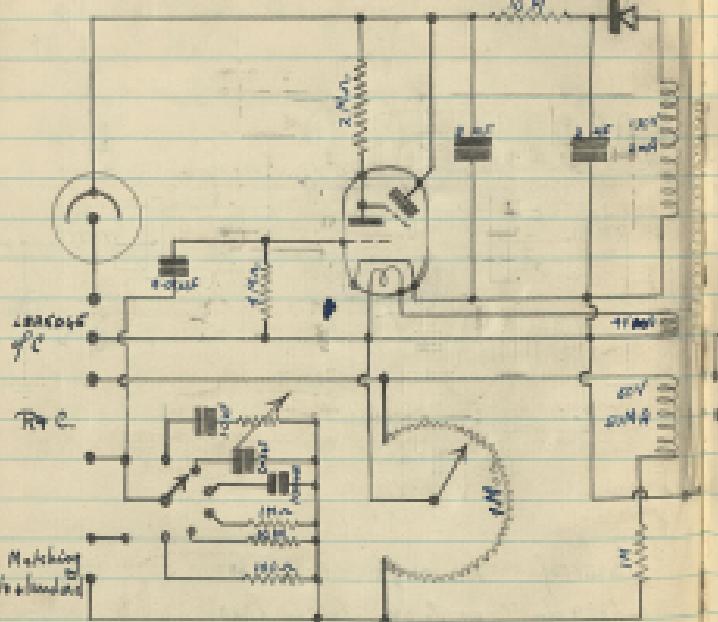Circuit of 120 Mc/s Oscillate
by 2 dipole we lesser tuning lines
L₁ is double wound $\frac{1}{2}$ turns
L₂ is $\frac{1}{2}$ chokes
C_{1,2,3} are R.F. Dipoles
C₃ is output Coupling C's.





Circuit of P.C. Bridge.

Signal generator.

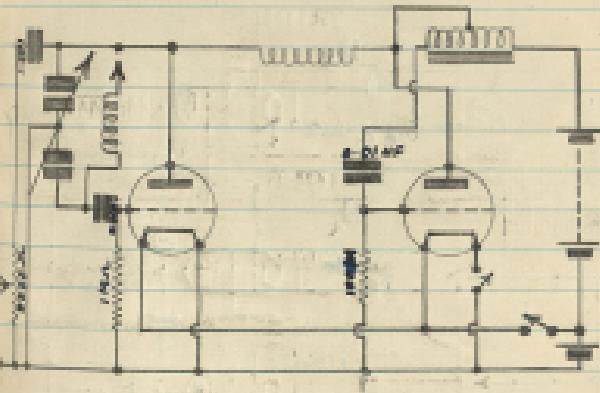

H 37

Circuit of typical T.R.f. universal set.

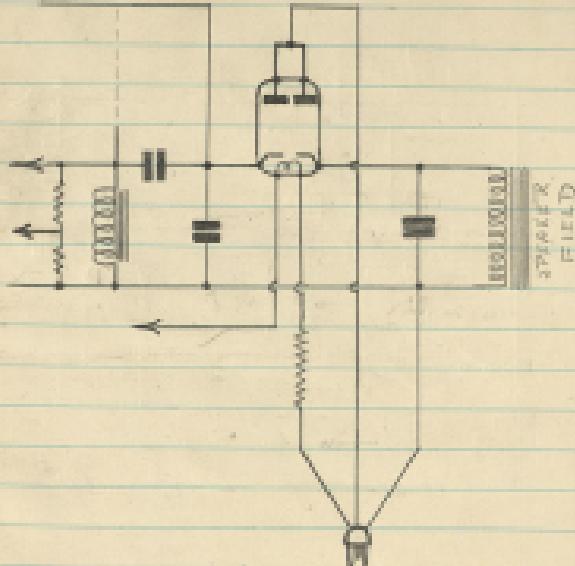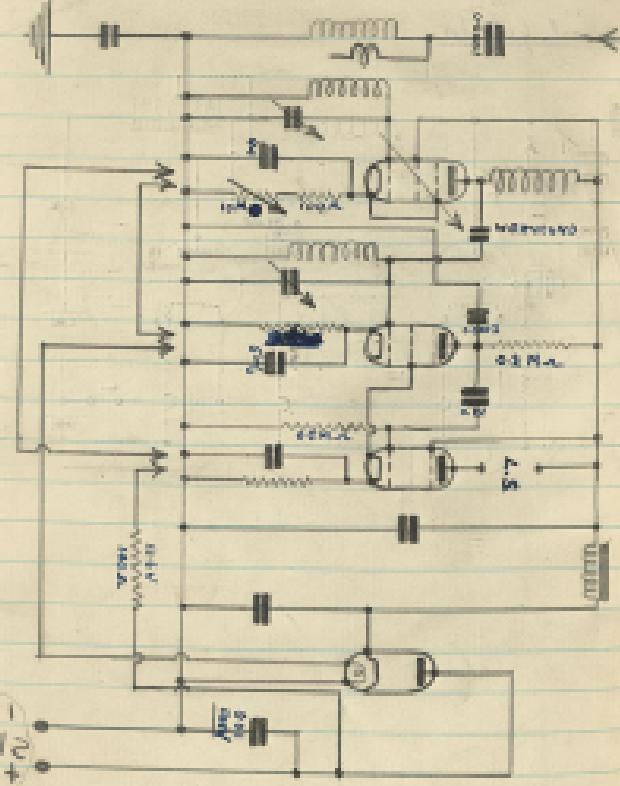

Let ω (instead of R) represent ω of R .

$$\begin{aligned} \omega &= \frac{V}{J_R} \\ &= \frac{V}{J_R g_m} \\ &= \frac{1}{J_R} \cdot \frac{V}{g_m} \\ &= \frac{1}{J_R} \cdot \frac{V}{\frac{R_L + R_o}{J_L + J_R}} \\ &= \frac{V}{J_R} \cdot \frac{J_L + J_R}{R_L + R_o} \\ &= \frac{V}{J_R} \cdot \frac{J_L}{R_L + \frac{R_o}{J_R}} \\ &= \frac{1}{J_R} \cdot \frac{J_L}{J_L + J_R} \end{aligned}$$


$$= \frac{1}{J_R + \frac{J_L}{J_R}}$$

$$= \frac{J_R}{J_R + J_L}$$

gegen J_R .

$$= \frac{1}{J_L + \frac{J_R}{J_R}}$$

Mathematical drawing in Bally's set

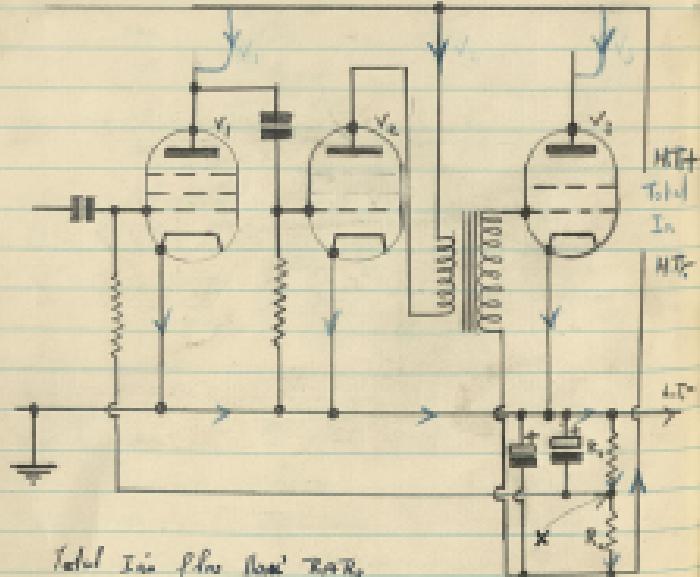

Total I_{in} plus load R_{load}

γ is equal to $1.5 - 1.6$.

Leaking factor may be calculated by large electrons
($12V, 25\mu A$)




a.

b.


c.
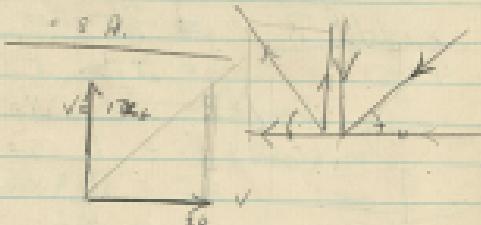
$$I = 1.2 \text{ A} / \sqrt{100+25} = \frac{400}{140.5} = 2.8 \text{ A}$$



$$\begin{aligned} a. \quad I_{in} &= \pi / R = 1.28 \\ b. \quad R &= \frac{120.8^2}{120} \end{aligned}$$

$$b. \quad I = 8 \text{ A}$$

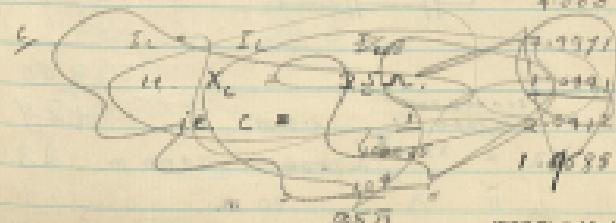

3

130 m T.L.A.

250.64 sec


3 > 1 m by same c. 200 minutes

$$\text{Total } R = \frac{200}{1} \\ = 20000 \Omega$$

$$\text{series } R = \underline{299,999 \Omega}$$

$$\text{half } R = \frac{0.1}{100} \times 10000$$

$$10^4 \times 10^{-5} = 1 \text{ ohm.}$$

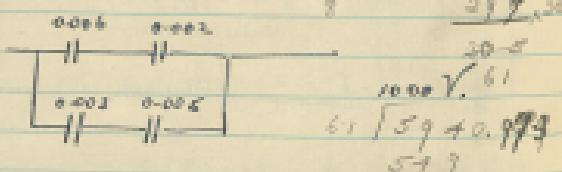

$$\frac{\text{percentage}}{\text{approx.}} = \frac{1.1}{1.0} - 1 = 12\%$$

$$I_A = \frac{20000}{10000} = 2000 \text{ m } \$30$$

$$I_A = 20 \text{ m } \underline{13.2}$$

of ~~unadjusted~~ a series of shunts.

27 - 18	$\frac{216}{220} = 98.2\%$	18
28 - 20	216 196	20
29 - 20	$\frac{216}{200} = 108\%$	20
29 - 60	$\frac{216}{60} = 39.5$	60
59 - 60	10 39.2	60

$$22 - 20 \text{ practical lab.} \quad \frac{22.4702 \times 2}{20} = 20$$

$$59 - 60 \quad \frac{109}{20} = 5.45 \quad \frac{66}{5} = 13.2 \quad \frac{109}{20} = 5.45 \quad \frac{66}{5} = 13.2$$

$$27 \quad 48 \quad " 98.5 - 39.13.2$$

$$59.5 \quad 59.5$$

$$77.5 \quad 59.5$$

$$7.8 \quad 29.5$$

$$86.1 \quad 89.0$$

$$98.5$$

$$100.0$$

(gi'-gi') (ga-ge + gi')

-gi-ge + gi-ge + gi'
-ge-ge - ge-ge - ge-ge

ga-ge + ge - 1
gi-ge + ge - 1

gi'-gi' (gi-ge + gi' - 1)
gi'-gi' (gi-ge + ge)

- 1 (gi-ge + gi-ge - 1)
gi'-gi' (gi-ge + ge)

- 1
gi-ge + ge G.E.B

had

Let d be the apparent distance of the cathode

$$V_c = I_a d.$$

$$\begin{aligned} V.A.F. &= \frac{V_c}{I_a} = \frac{d}{g_a + g_g + g_c} \\ &= \frac{d}{\frac{2d}{3}} = \frac{3}{2} = 1.5 \\ &= \frac{d}{d} = 1 \\ &= \frac{3}{3} = 1 \\ &= \frac{3}{3} = 1 \end{aligned}$$

~~3m - ga-ge + ge / gi-ge~~


- 1 - 1
gi-ge 3m

- 1 - (ga-ge)
3m (ga-ge + ge)

- 1 -
~~3m / (ga-ge + ge) gm~~

(language - 1)
language 2


language - 1
language 2

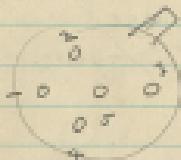


24+ holes.

1. Grid control.
5 cathode.
1 or 5.


Top. anode
2 holes

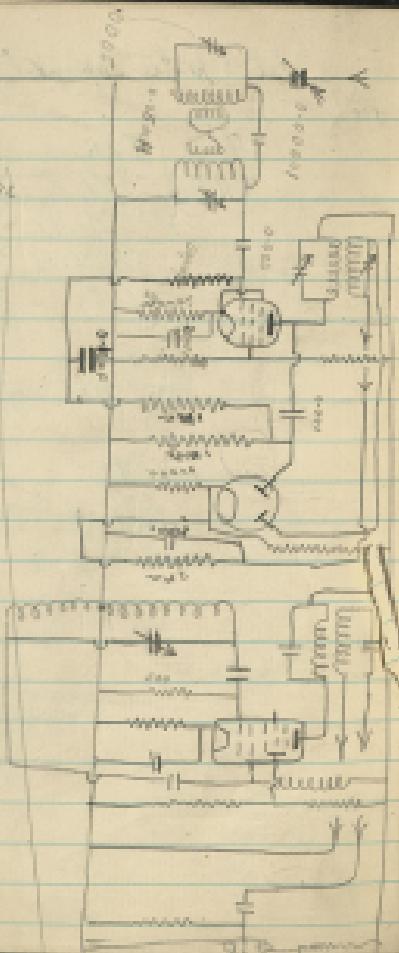


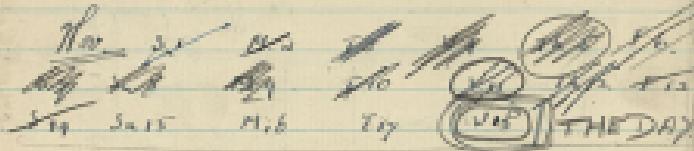out on no yet get off at 200
not pass too far not yet get 142
Aug 7 20 (3-21) on intermediate station





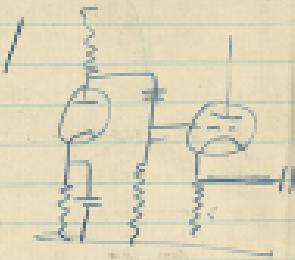
B.O. C.R. cut-off.
37 M.V. 05 M.H. feedback line.
no feed back.



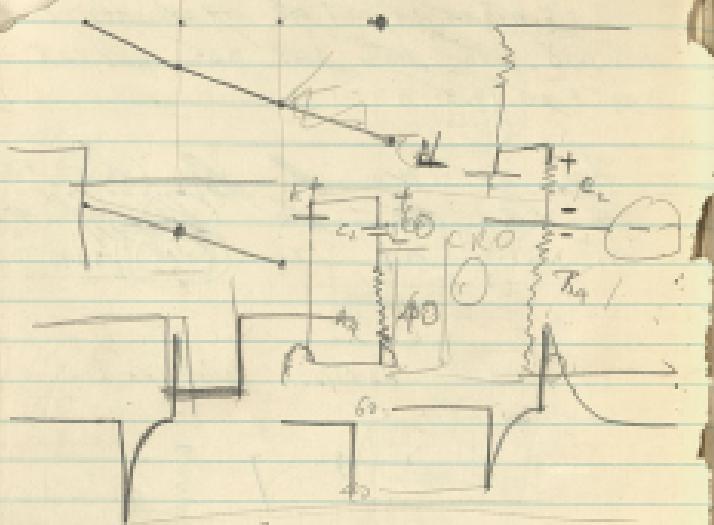

- 1) $E_a = 120V \quad C_1 = 90 \quad R_1 = 60$
- 2) $E_a = 100 \quad C_1 = 90 \quad R_1 = 10$
- 3) $E_a = 150V \quad C_1 = 90 \quad R_1 = 60$

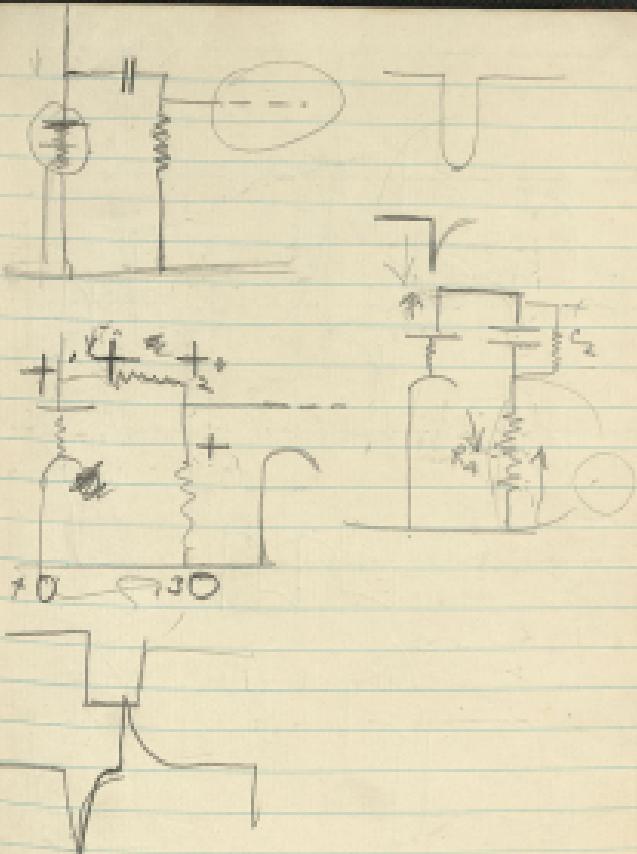

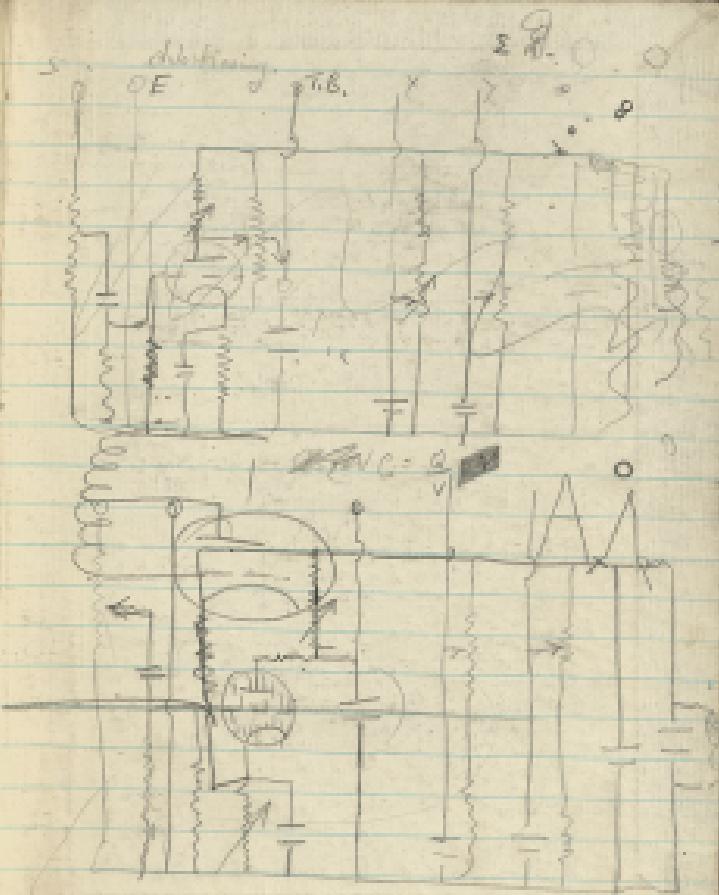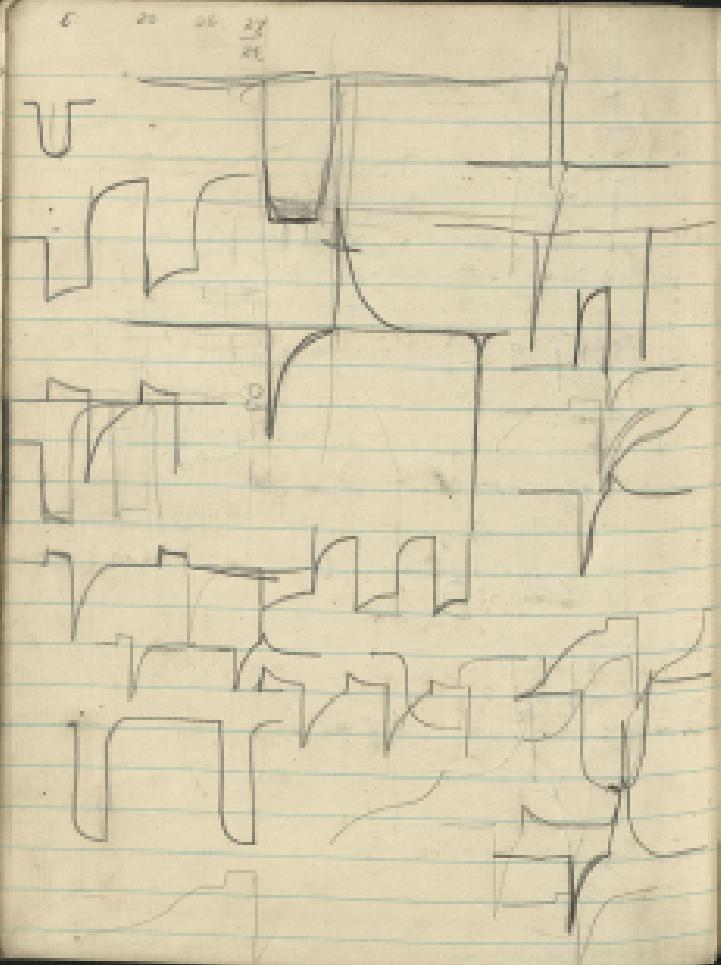

ANNE V. DAVIS