

A.B.C.
SCIENCE NOTE BOOK

Name PT. J. ROBSON, T.R.O.C.

RADIO MECHANICS

Class

A.B.C. Co.,

20 West Regent Street.

Expt. 10. To study the effects due to various combinations of cells.

The circuit as shown can be varied with a voltmeter & a spring switch. The various combinations used are shown. The cell used were accumulators of approx. 2.2 V.

1. Voltage of cell = 2.2 V.

2. Two in series

$$V = 4.4 \text{ V}$$



3. Three in series.

4. Two in parallel

5. Three in parallel



$$V = 6.6$$



$$V = 2.2$$



$$V = 2.2$$

6. Four in series
parallel.

7. Two in opposition

8. Three in opposition



$$V = 4.4$$



$$V = 0$$



$$V = 2.2$$

with lines on
left side.

Conclusion ?

EXPT. 13 To show that $I \propto 1/R$ provided E is constant.

The circuit was arranged as shown, four equal resistances being used in different functions, viz.
one, two, three & four in series & four in parallel-
series.



I in mA	Resistance	
128	one	$\times 1 = 128$
65	two in series	$\times 2 = 130$
43	three ———	$\times 3 = 129$
31	four ———	$\times 4 = 124$
130	four in series- parallel.	$\times 1 = 130$

Within the limits of experimental error these results are identical. This shows the product of $I \times R$ is constant. $\therefore I \propto 1/R$. ✓

EXPT. 14 To study the relationship between $I \times V$ of various resistances.

The circuit as shown was arranged with fixed resistance of three 50Ω , 100Ω , 200Ω , 400Ω , 800Ω , 1600Ω , 3200Ω , 6400Ω .
The rheostat was used to vary the volts drop across the resistors & thus the current. But it is better to give several readings. The current being always the same, $I \propto V$ if R is constant. i.e. Ohm's law is true.



For graph see i. at end of book. ✓

EXPT. 1D. To study the relationship of the I & V of a lamp.

The circuit was as shown & as the rheostat was progressively moved, different readings of voltmeter & ammeter were taken. The correct reading was taken before the voltmeter circuit could be closed.

The graph showed that the resistance increased with greater current i.e. with increased temperature.




See graph on p. 10 at end of book.

V

EXPT. 1E. To find the resistance of various radio components.

The usual circuit for measuring resistance was arranged with a c. r. tube as an unknown resistance.

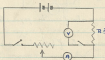It should be noted that very erratic results occur when the resistance is very high. This is due to the resistance of the voltmeter being comparatively low. It should be as high as possible & in fact an electrostat is quadrant electrometer, with infinite resistance would be more accurate.



Low frequency tube.


<u>I in Amperes</u>	<u>V in volts</u>	<u>R in ohms</u>
0.0029	2.1	1051
0.0037	2.6	789
0.0035	2.2	915
0.0034	2.1	911
0.0033	2.0	908

The average resistance = 911.78 Ω

EXPT. 15

To measure resistance & compare the results with the estimated value.

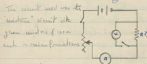The circuit used was the "resistance" circuit with given resistors of 100Ω each in various formations. The values of the formations were estimated & compared with the average result by experiment.



i. The average value of resistor = 99.9Ω : the calculated value = 100Ω

ii. The average value of two in series = 200Ω : the calculated result = 200Ω .


iii. The average value of three in series = 300Ω : the calculated result = 300Ω

iv. The average value of four in series-parallel = 99.9Ω
The calculated result = 100Ω .

V

EXPT. 16 Measurement of high resistance by the "Megger".

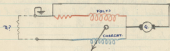The megger consists of a generator hand by a handle, the measuring part is two coils set at right angles & arranged to turn in opposite directions. One, the voltage coil has a high resistance in series with it. The scale gives direct readings of resistance.



i. Value by megger = $1,000,000 \Omega$: Estimated value = $1,000,000 \Omega$

ii. Value by megger = $500,000 \Omega$: the estimated value = $500,000 \Omega$

iii. Value by megger = $200,000 \Omega$: Estimated value = $200,000 \Omega$

iv. Value by megger = $100,000 \Omega$: Estimated value = $100,000 \Omega$

EXPT. 14. To show that $R \propto l/a$.

Current diagram?

I found carrying three resistance wires, uniform in length & cross-sectional area & which could be connected in any way at will by copper links, was in series with the "resistance" circuit. The resistance was found with one, two & three wires in series. The results were in simple proportion 1, 2 & 3. With one, two & three in parallel the resistance was halved & thirded. This showed that $R \propto l$ & also $R \propto \frac{1}{a}$ i.e. $R \propto \frac{l}{a}$.

In series.

I	E	R	
0.66	1.22	$\rightarrow 1.9 \div 1.9 = 1.0$	1 wire.
0.43	1.6	$\rightarrow 2.72 \div 1.9 = 2.0$	2 wires.
0.32	1.8	$\rightarrow 5.80 \div 1.9 = 3.0$	3 wires.

In parallel.

I	E	R	
1.10	1.10	$\rightarrow 1.0 \div 1.9 = \frac{1}{2}$	2 wires.
1.30	0.86	$\rightarrow 0.62 \div 1.9 = \frac{1}{3}$	3 wires.

✓

EXPT. 14i. To study the relationship of P.D. & resistance.

The circuit was arranged as shown with four equal resistances. Voltmeter V_2 can be used to find the P.D. across first one, then two & three of the resistances.

So and since the P.D. was proportional to the resistance showing that Voltage drops evenly in a resistance.

P.D. across 4 resistances by V_1	$= 2.05V$
1	$V_2 = 0.50V$
2	$= 1.00V$
3	$= 1.50V$
4	$= 2.00V$




EXPT. 18. A further verification of $P.D. \propto R$.

In the experiment the four resistors were replaced by a uniform potentiometer wire.

A graph, shown at the end of the book iii, was found to be a straight line.

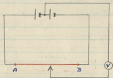Missed purpose
10. $R \propto P.D.$ of Exp.



✓

EXPT. 19 To find the voltage drop in leads.

The circuit as shown before was arranged. The current was varied by the rheostat in order to give several voltage readings. The leads between the voltmeters were of high resistance in order to represent long transmission lines.


The graph (iv) shows that the P.D. in the leads is proportional to the current consumed.

✓



EXPT 12 Measurement of resistance by the "Bridge Method."

This instrument is a bridge arrangement of resistances in conjunction with a meter. It is used as a meter but also utilized to bridge the current coil is used as the galvanometer of measuring bridge arrangement so that when the bridge is balanced no current flows i.e. the needle reads infinite resistance. Tappings from the three fixed resistances are provided for convenience when measuring resistance.

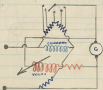

Range?

EXPT 13

To measure the resistance of a set of resistors & compare the result with the cat-included value.

The "resistance" circuit was used with the network. Several values were determined & the mean taken, by adjustment of the rheostat.




The calculated value is 20 ohm

The average value by experiment
= 28.68 ohm Poor

EXPT 2A. Matching load to source.

The circuit was arranged as shown in order that an appreciable internal resistance's effect should be felt, a $10\ \Omega$ resistor was put in series in order to make an artificial internal resistance. The load was varied & the output plotted against resistance. The curve reached a maximum at an external resistance of $10\ \Omega$, the equivalent of the internal resistance. Thus for maximum output the load resistance must equal the internal resistance.

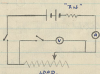


See graph use γ at end of book.

EXPT 2A. To show that when equal output is obtained from different circuits, the energy is equal in each.

The four lamps were used in the circuits in series, then parallel & series-parallel. In each case the rheostat was varied until the lamps glowed. This ensured that the output was constant.

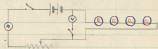The voltage of each arrangement was found & within limits of experimental error they were identical.



	Series	Series-parallel	$V = 0.81\ \text{volts}$
parallel	0.96	0.90	0.864
series	0.274	0.40	0.816
series-parallel	0.95	0.86	0.857

The average voltage = 0.859 V.

EXPT 5075B To examine the magnetic field round a straight & a coiled conductor.

The circuit was assembled, the leads were of thick copper in order to obtain maximum current. With a known compass the configuration of the magnetic field was found in both the coil & a straight part of the circuit.




Magnetic field round a straight conductor carrying current.



EXPT 5075D To examine the magnetic field due to a coiled conductor.

The solenoid was first used with no core i.e. air core, & the compass needle was unaffected by its field until it was quite close to it. There was no field when the current ceased to flow.

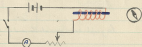With steel & soft iron, by virtue of their permeabilities the compass needle was affected at a great distance, more so in the case of soft iron. When the circuit was open the steel retained a fair amount of magnetism but the soft iron lost practically all.



SEPT 28 To examine the terminal P.D. of primary & secondary cells with load.

The circuit as shown was working at first with a dry cell & then an accumulator. The load was varied & the terminal volt. determined. With large load the terminal volt. of the dry cell were very low showing that this type of cell should not be used for large current. The accumulator with a low internal resistance gave a good performance.



See graph on pg at the end of the book.

The irregular wave for the dry cell is caused by the recovery of the cell from polarisation.


SEPT 28 To examine the field of a solenoid.

The solenoid was connected as shown. With a compass & a piece of iron wire outside the solenoid & another inserted between the coils inside the solenoid, since the poles were generated opposite ends the repulsion occurred. When a paper was placed half in & half out of the solenoid it was attracted to the center where the magnetic field is strongest when the current is switched on.



EXPT. 4C To study the effect of overloading of radio components.

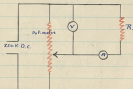The circuit was as shown. From the given ratings of the component & its resistance, its working voltage was calculated. By the potentiometer half load, full load & overload were applied. The component was quite cool with half load, comfortably warm on full load but unbearable hot on overload. Overload may then cause a resistance to heat up & may cause serious damage in a radio set.




EXPT. 4D To examine the "Seebeck Effect".

A thermocouple was constructed from thermopile consisting of constant metal (iron) & copper. When the junction was heated an e.m.f. was found between the ends of the wires & caused a current to flow thru the meter. The principle can be applied to measure T.M.S. values of temperature but due to the heat being proportional to I^2 the scale is a square law scale. The flow of electricity is from iron to copper. It should be noted that the converse is true & is called the "Peltier Effect".




EXPT. 60. To examine motor effect & also Fleming's left hand Rule as it is.

The following circuit was arranged. Current was taken from a cell via a reversing switch & a spring switch to two parallel copper rods fixed to a board & between the poles of a powerful, permanent horseshoe magnet. A copper wire was free to rest on the two fixed rods. When a momentarily large current was passed the latter moved in a direction determined by the field & direction of current. These were varied & Fleming's left hand rule for motors was found to be true.

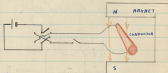

EXPT. 61. To examine the hot wire meter.

The circuit was as shown. A constant wire heated & a pointer was attached to a weight was hung between two wooden supports. The deflection was read off on a linear scale. The graph of current^2 against deflection was a straight line due to deflection being proportional to heat which is proportional to current^2 . This shows that the scale of an instrument working on this principle is a square law scale. The chief advantage of such an instrument is its ability to measure A.C.

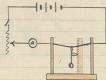

EXPT. 50

To find the relationship between the torque of a moving galvanometer & the current flowing through it.

A moving iron (attraction type) galvanometer was in series with a r.p.s. variable & a rheostat. The deflection on a linear scale was noted, with different currents.

A graph of deflection against current was drawn.

The latter was a straight showing that the deflection was proportional to current. That is, the scale of a direct reading ammeter could be a square law scale.

The experiment was repeated but the pointer was brought back to zero deflection by the addition of weights. The graphs of the two methods are shown at head of the book at iii.



EXPT. 51

To examine a moving iron galvanometer (continued)

This consisted of a coil which was capable of carrying a large current. But, a little bit of iron, was a current of soft iron, another blade of soft iron was arranged to swing with a pointer over a scale. The effect was to allow this blade to be repelled. Damping was effected by a spring. The scale was square law, until the distance between the two poles was appreciable when an inverse square law was indicated for this. The scale at the end of the range was rather cramped due to the damping of the spring. The expression m/r^2 explains the shape of the scale.



EXPT. 7D

To study the build of t.m.f. with field of a shunt generator.

74.

To study the external characteristics of a shunt generator

74.

To study the external characteristics of a compound generator

75.

To study the external characteristics of a series-compound generator.

A generator with variable connections was coupled to a prime mover. The generator was connected as a shunt machine & with no load the terminal v.t.t. was examined with varying field.


With a fixed field the terminal v.t.t. was examined with varying in the case of a shunt generator, & compound generator, both cumulative & motor wound. The graphs are at the end of the book.

Expt 7D


EXPT. 5H

To test a contactor or relay.

An electric bell was placed in a circuit as shown. The current was varied until the armature just moved to the coils. Residual magnetism held it there with the help of the current. The armature remained so until the current was drastically reduced. The case is since the armature moved at 0.05 A returned at 0.01 A .

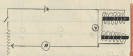


EXPT. 6E. To examine a motor-sender.

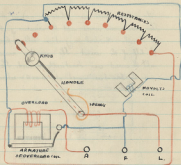

As the handle is moved, resistance is taken from the circuit & the no volts coil energized. If the current stops, due to a short circuit of the no volts coil, the handle flies back. The overload release affects the short circuit of the no volts coil when current flows.

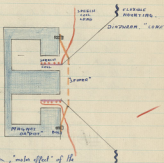
EXPT. 6E. To examine a many coil speaker.



The interaction, "motor effect" of the magnetic field which may be that of a permanent magnet or an electro-magnet & the fluctuating field of the speech coil causes the speech coil to vibrate, producing sound. The spider supports the spring arrangement for the speech coil.

EXPT. 2A To examine Electro-Magnetic Induction.

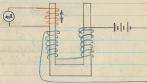A coil of wire to which was attached a centre zero millimeter was moved over one pole of an energized electro-magnet. Deflecting e.m.f. was induced in the coil & a vol. as in the opposite direction was obtained on taking off the coil. The mag. rate of this was increased by increasing the speed & also using a larger coil.





EXPT. 2B To study meters in operation.

The circuit was arranged as shown with a rotary reversing switch. The moving coil ammeter tried to show the A.C. but gave up after reaching a high frequency the moving iron meter, due to its non-polarizing frame, was able to give the R.M.S. value of the current. It was noted that when the core was removed from the transformer the e.m.f. & hence the current in the secondary circuit were reduced.




The circuit was as shown. When the key S_1 was depressed the immediately rose to the value of the cell current thru R_1 while R_2 due to the retarding action of the inductance of the primary winding of the transformer took some time to reach the maximum. Meanwhile a current (emf) was induced in the secondary in proportion to the rate of change of the primary current. When the circuit was opened R_2 & R_3 took some time to reach zero while R_1 reacted it immediately. The current in transformer travelled thru R_3 & was shown on that in with inductor.

A graph of the currents with time is appended. The other half of the circuit again shows the decay of current for when S_2 is closed S_1 is kept off immediately while S_2 takes some time. This again is due to the inductance of the coils.

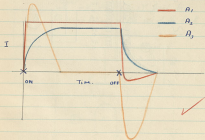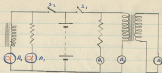

EXPT. 8.2 To show that induced E.M.F. is proportional to flux-linkage.

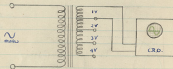A C.R.O. was connected as shown. With a fixed primary & equal tapping of the secondary it was found that the induced e.m.f. was proportional to the amount of secondary windings.




EXPT. 19 A3B To examine the anode current with varying grid bias of valve 635 the anode current with varying anode voltage.

The circuit as shown in varying E_g was made to control I_a . This was done for the values of E_a , 40, 96 & 70V. The values T.B. 282 & 120.

With the grid bias constant reading of I_a with varying E_a were taken for both values with 0V, -1.5V & -2V grid bias.

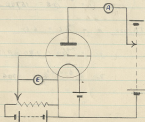The graphs are at the end of the book p. 44



Expt. 19C To calculate the constant values of a motor.

R_a , μ & β for the two values were calculated from the results of Expt. 18.

$$\text{T.B. 200} \quad \alpha = \frac{100/100}{26/100} = \underline{15.20}$$

$$\beta = \frac{100/100}{26/100} = \underline{1.029 \text{ m/V}}$$

$$R_a = \frac{100/100}{100/100} = \underline{15.790 \text{ m}}$$


$$\text{T.B. 100} \quad \alpha = \frac{100/100}{16.6} = \underline{6.47}$$

$$\beta = \frac{100/100}{16.6} = \underline{1.90 \text{ m/V}}$$

$$R_a = \frac{100/100}{16.6} = \underline{3.672 \text{ m}}$$

Expt. 19D To study the Cuf of a D.C. generator, separately excited, under varying excitation.

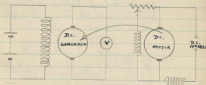The generator was driven by an electric motor. With the field current constant, the terminal P.D. was noted at various speeds. Then with the speed constant, the P.D. was taken with a varying field. The graphs are ~~attached~~.



The bend in the second graph is due to the saturation of the iron in the field magnets.

The graphs show that:-

$$E = If \quad \text{ie} \quad f \text{ since } f \propto If$$

$$E \propto I$$

$$\therefore E \propto Nf \propto NI$$


Expt. 6.2 To examine the action of a motor-shunt & field regulator.

A motor was connected as a shunt motor as shown. With the current controlled on, nothing happened. As the resistance was taken off the armature circuit the motor speeded up. As the resistance was put off the field circuit the motor speeded up till it reached an up throw limit, then further reduction of resistance caused it to slow down. This due to there being less back e.m.f. & therefore more effective voltage across the armature. The terminal P.D. of the armature was seen to increase.



Expt. 6.3, 6.4, 6.5 To examine Induction

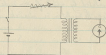The circuit was as shown. When the switch was closed an e.m.f. was induced in the secondary coil & when opened an e.m.f. in the opposite direction. The rate of change of flux considerably increased this effect. The value of the induced e.m.f., was seen to increase the e.m.f. induced.




The "flux linkage" was affected by moving the solenoid. It was seen that the e.m.f. depended on the speed of movement. Again the flux linkage was affected by moving the primary coil in relation to the secondary with a constant current. The same effects were noted.

The primary was replaced by a bar magnet. Again the amount of flux & the rate of cutting lines of force was seen to govern the size of the induced e.m.f.

EXPT. 20 To examine a transformer.

The core was laminated & built up as shown. The primary windings were of thick copper wire & consisted of comparatively few turns. It was capable of carrying high currents. The secondary coils were thin & a great number. In this small transformer the laminations were insulated by means of "iron oxide", rust. but in larger size the insulation is mica, etc.

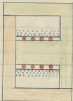

EXPT. 20-2 To study the relationship of primary volts & current to secondary volts & current & the turns ratio.

The transformer used had 2500 turns in the primary winding & 2500 in the secondary. A.C. source supply of 200 V. was used & the output was noted to be 411 V. which agreed with the volts as calculated from $V_1/N_1 = V_2/N_2$.

With varying loads it was found that the currents were in inverse proportion to the turns ratio. A slight current in each case was noted but this was for the losses in the core, eddy currents, & heating losses etc. $I_1/N_1 = I_2/N_2$



To examine the self induction of a coil.

The coil was connected in series across a 200 v. a.c. supply. The voltmeter across the coil was varied by means of the rheostat at 2 different values of P.D. across it current thru' the coil. This was repeated with 1, 2, 3, 999, 1000.

The graphs are shown in fig.



To examine condensers

1. Roll of waxed paper between two plates of aluminium foil, given large, fixed condenser.
2. The roll used in a tubular, small type.
3. mica dielectric, 2 half plate made in a tubular container, small fixed type.
4. Variable condenser with aluminium plates, cone-shaped, moved on a common spindle in between fixed plates. Also was the dielectric.
5. The same as above but with tubular or mica dielectric.
6. Electrolytic condensers. Vide Phys. Notes


EXPT. 9D ? 9E

To charge & discharge condensers.

The condenser were used, which could be connected in parallel at with 250 Volt. D.C. was put across two thin resistance. When the P.D. was 250 V. the charging stopped. The charging was slow due to CR (the time factor) being large (Resistor). The condenser were short circuited (no resistance) & CR was too small so that the discharge was quick & resulted in a large, noisy spark.

When the condensers were discharged then the resistance it both was changed for the charge to disappear.

graphs?

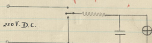EXPT. 9D

To examine the leakage of a condenser.

The condenser was charged & left. The Electrostatic Voltmeter showed that the condenser discharged only very slowly showing the danger of leaving charged condensers about.

EXPT. 9E

To charge further condensers from a condenser.

A set of two further condensers were charged from the circuit. The P.D. was seen to decrease as some of the charge left to charge the second set. With the charging circuit closed, the charging again finished at 250 V.


P.P. 4/10/52

EXPT. 21. To construct a Hertzky Oscillator.

The circuit as shown was arranged. The first value letter only was used. The grid leak 100,000 Ω was deliberately made large. In order to obtain "sparking" the graph of plate current against the setting of the condenser is shown graphically xiv.

When the R. f. choke was started no "feed-back" was available in the a. c. circuit & so the plate current was to a minimum. This also occurred when the bias on the grid was cut off by shorting the grid leak. When the tuning condenser was shortened the current again increased owing to the signal stopping.


The coil used was an "all-purpose" coil as shown

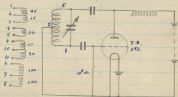

EXPT. 21A. To modify the Hertzky Oscillator as a Transmitter.


The Hertzky Oscillator was arranged with series modulation as a Transmitter.

It was noticed that under motion caused the frequency to drift.

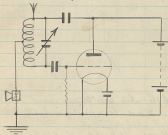

EXPT 22. To modify the Hartley Circuit as a Receiver with Reaction

The circuit was as shown.

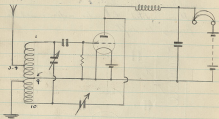

22A. With the cathode heater terminals reversed i.e. the grid back to $L.T. + ve$. the reproduction was slightly louder due to the small initial grid current.


22B. The R.F. was bypassed to earth from the cathode & was thus unable to supply any "feed-back" by developing a voltage across the R.F. coils.

22C. With the aerial connected to pin 1 the capacity of the aerial was in parallel with the tuning condenser & the result was that the stations appeared in different

orientations of the tuning condenser. The selectivity also became very bad.


With a small condenser (0.0005) in series with the aerial the aerial capacity was reduced & thus all the bad effects were offset.

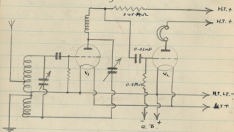EXPT. 22 The Pushing Reverser with stages of Rf. amplification
with R.C. coupling



The grid bias of V_2 can be altered causing grid current to flow at a time & cut-off (distortion) at a high bias. This gave rise to distortion. I_a was also altered.

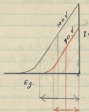As the anode voltage was varied the grid capacitance was decreased & if the signal was strong, distortion took place. I_a also altered.



A Rf. modulated to 100 cps. was introduced into the circuit. The Potential between grids & cathode of V_2 was noted on the C.R.O. & also between anode & cathode. The stage gain was the fraction of the two. $D \approx 6$. The voltage was noted to be out of phase.

$$\Delta E_g \approx \Delta I_a \approx 1/\Delta E_a$$

$$\therefore \Delta E_g \approx 1/\Delta E_a$$

i.e. as the grid was made more +ve, say, the anode vol. dropped.


EXPT. 24 To investigate Phase Inversion.

The circuit was as shown.

When a +ve signal is applied to V_1 , i.e. the grid is made more +ve. I_a rises & thus the P.D. across the anode load. The anode potential is decreased, & since this potential is applied, via the potentiometer, to the grid of the second valve, the grid becomes more -ve & thus I_a reduces & also E_a increases.


When a change is made in grid potential anode potential varies in an opposite sense.

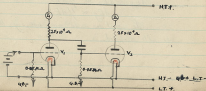When only one grid line is altered, I_a varies & this in effect is fed back on the H.T. supply changing it. The resultant change in P.D. across the internal R of the H.T. supply affects both the valves E_a 's & thus their I_a 's.



EXPT. 25 The Symmetrical Multi vibrator.

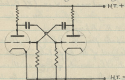This circuit was arranged. The C.R.D. was used to study the wave forms of the voltage variation between the two anodes, the anode & cathode & the grids & cathode of either valve. By its variations an oscillation having the wave form as shown was produced, the frequency being determined by the values of C & R in full reference to the working see theory notes.



EXPT. 26 The Blocking Oscillator.

So full notes in this circuit are flying notes.

Different values of condensers were used, the smaller caused no "spray" & the large ones gave "spray" at different resonance frequencies.

$$R_1 + R_2 = 20000 \Omega \quad R_{12} = 170 \Omega$$

$$R_1 = 20000 \Omega \quad C_1 = 0.001 \mu\text{f.}$$

$$R_2 = 20000 \Omega \quad C_2 = 0.001 \mu\text{f.}$$


The values used were V_{cc} (Rf Pentode)

The traces as given by these values are shown later.

EXPT. 26 The C.R. shaping circuit.


The impulse from the Blocking Oscillator is improved on the grid of the "cut-off valve" via the C.R. shaping circuit. This consists of a very small condenser & a large resistance in series giving a low time constant. When there is a down ward change in E_c the condenser charges & then discharges when there is no change in E_c . This is made possible by keeping E_c very low. If it is high nothing happens to the C.R. shaping circuit because no an. ordinary coupling. During the change of E_c to 10 a maximum the C charges, the time is an opposite sense. The C.R. O. traces

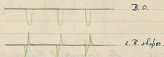show this & it can be seen that the C.R. shaping circuit changes the impulses from B.O. into a - or + pulse with the same R.f.



EXPT. 27 The "cut-off" valve.



The impulses from the C.R. shaper are improved on the grid of a pentode which is biased into cut-off so much that only the tops of the original impulses affect the valve. These show as "kicks" in E_c of this valve in a - or + direction. It can be seen that the shape of the impulse from B.O. & the "cut-off" valve are the same shape but the P.D. is much lower in the latter case although R.f. is constant. With these traces on the "cut-off" valve I acted as an ordinary amplifier.

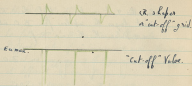

EXPT. 28

The Symmetrical Multivibrator.

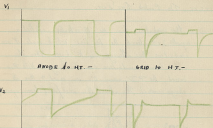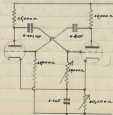This works as the Symmetrical M' vibrator with modifications in biasing & the coupling giving different wave forms.



ANODE to H.T. -

GRID to H.T. -



The wave forms may be modified by alteration of the variable bias & grid leak.

The waveform was almost square, the desired waveform! The bias V_{g1} is used to "cut off" the tubes. R_{g1} modifies the waveform by altering the C.R. constant & connects a sort of "cut off" when it shorts the grid to earth. V_{g1} is affected by the cutting off of V_1 , which valve experiences a great change in I_a .

Since V_2 grids directly connected to the cathode via R_{g2} . There is no C.D. between grids & cathode so neither has R_{g2} is varied.

Expt. 4. The Purple Tree Toad

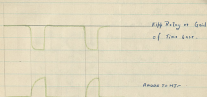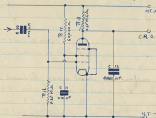The impulses from the M. vibrator applied a negative -ve bias to the base bias which made it non conductive thus allowing C_{12} to charge. When the valve became conductive C_{12} discharged. With R_{12} varied the P.D. across C_{12} was varied & thus its charge varied. This altered the wave form (became spiky)




The impulsive & slope is controlled by R, D & ω_2 .
 whilst the a.f. is controlled by the Kipp-Ruley which is
 controlled in turn by the B.O.

With all the conf. made working together. The diff. only
was adjusted to give a desired effect with no overloading
etc. The cut-off valve was turned to cut off.

The 'j' of the arrangement was controlled by R. & B. R. 26 controlled the Landing & was not one not released.

R_{in} , R_{eq} & R_{out} were left unchanged. R_{in} controlled the amplitude & the shape of the output waveform.

SYMMETRICAL ACTIVATION

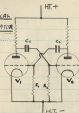


Suppose V_{g1} changes in -ve sense.
- E_{a1} rises. - This is transmitted
via $C_2 + R_1$ to V_{g2} - V_{g2} rises.
(or more) - E_{a2} falls - This drop
in E_{a2} is transmitted to V_{g1}
via $C_1 + R_2$ - V_{g1} becomes still more
-ve etc. etc. until V_1 is
"biased" to "cut off."

Whilst V_1 is ~~being~~ becoming "biased" V_2 is rising to saturation
with V_1 an inhibitive feedback from V_2 to V_{g1} causes the
system release at a rate governed by the time constant
of $C_2 R_1$.

As V_{g2} potential $\rightarrow 0$ - V_2 becomes conductive & the
amplifying properties of both valves are reestablished with
 V_{g2} rising in potential (more -ve)

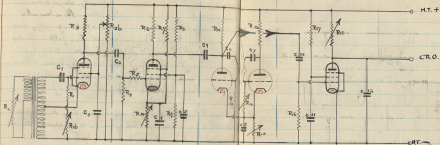Feedback now takes place in the reverse sense & the voltages
build up until V_1 is saturated & V_2 "biased".




Blocking Oscillator

CTR Shaping Circuit
& Cutoff Valve

Mechanical Frequency
or 60PP Relay

Triode
Time Base

Voltage Levels of B.O. + C.R. 3 Lamps

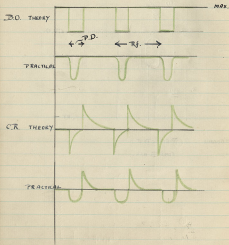

By suitable choice of circuit constants, the ratio $P.D. / R.f.$ may be made as high as 1/10 (i.e. $P.D. = R.f./10$). The variable bit of the B.O. controls the resonance frequency. It is sliding contact as a fine control on R.f. The P.D. across C_2 rises as I in a.c. When R_2 is decreased the I thru' R_2 is drawn from the a.c. circuit & P.D. across C_2 becomes less. The change in C_2 is less & balancing is no longer linear but R.f. is greater.

C_2 & R_2 constitute the C.R. sloping circuit. The time constant of these is very small (C_2 & R_2 are small & R_2 is a.c. circuit). The condenser charges during B.O. and discharges during C.R. period of no change, recharges in opposite sense while B.O. & E_a is on its upward excursion & discharges during reverse period. The C.R. circuit shapes the P.D. & inserts the over form. i.e. charges a saw pulse into a positive pulse.



The Cut-off Value.

This is a pulse which is immediately positive by R_{2max} (R_2 is also small not functioning). Cut-off = 0. In = 0 line. R_2 is a "bleeder".

The tip of the pulse from C.R. sloping circuit affects the line & the pulse becomes momentarily positive thus producing a negative pulse of E_a which has a duration of very


So of the whole of the wave pulse from C.R.

Voltage across of Cut off Valve.

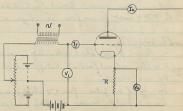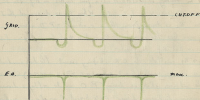

EXPT 2.1 Thyristor feed back.


The circuit was as shown.

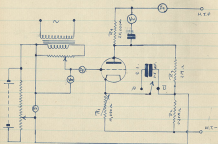

With the circuit as shown there was NO D.C. feed back.
~~but~~ ~~the~~ ~~current~~, i.e. A.C. feed back at 2 as feed back.
 The waves are shown in 86.

1. I_a with change in V_g - no feed back.
2. I_a with no feed back.
3. I_a with D.C. feed back (absence of cut-off - shallows slope.)
4. I_a with A.C. no feed back - normal valve behaviour.
5. I_a with A.C. no feed back - normal valve behaviour.
6. I_a with A.C. no feed back - normal valve behaviour.
7. I_a with A.C. no feed back - normal valve behaviour.
8. I_a with A.C. no feed back - normal valve behaviour.
9. I_a with A.C. no feed back - normal valve behaviour.
10. I_a with A.C. no feed back - normal valve behaviour.

5-11-32 The Cathode Follower

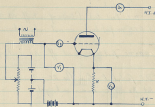

R was in turn $100k$, $100k$ to $100k$ ohms. To effect the high output line caused by R the balance & potentials were incorporated in the circuit, in order to track it off.

R ohms	V_1	V_2	Dist	$R_{in, max}$	V_1	V_2	Dist.
	28V	25V	3V		45V	41V	4V
20	28	25	3	10	41.5	38	3.5
40	28.4	25.4	3	20	39.4	36.4	3
60	27.8	24.8	3	30	38.0	35.0	3
80	27.0	24.0	3	40	37.5	34.5	3
100	26.0	23.0	3	50	36.0	33.0	3

In fact to cut off at a high neg. line E_g .


Resistor	V_1	V_2	Dist.
	40V	37V	3V
20	38	35.5	2.5
40	36	33	3
60	34	31	3
80	32	29	3
100	30	27	3

It is seen that the feedback is not 100% effective. There would be no difference between V_1 & V_2 .

The feedback out to in was in the ratio of 2:1 so that C.F. diminishes the signal. The advantage is that it is an excellent comp discriminating matching device, if the output is taken from R .

It will be seen that the value (μ) of R has no apparent effect on the results. This is because the effective R is $1/\mu$.

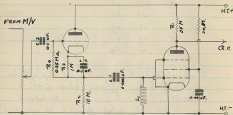
Expt 12 The L.C. shaping circuit in triggering circuit.




During the downward portion of the M/V trace E_a charges & applies a negative charge to the grid of the amplifier, where E_a rises. When the M/V trace is already C_1 discharges then L_1 whose inductance produces a back e.m.f. which tries to make the grid very positive i.e. E_a falls. I_g , however, damps this effect. C_1 & L_1 produce very heavily damped oscillations.

During the upward excursion of E_a of M/V. C_1 charges in the opposite sense & tends to impress a very positive charge on the grid. I_g again damps this. When the M/V. becomes positive C_1 discharges

The discharge produces oscillations in L_1 & C_1 very heavily damped, of course.

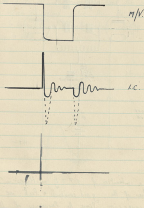


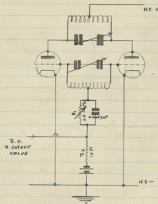Expt 29. The P.P. Squeezing Rf. Oscillator.



This is a combination of P.P. & oscillator in Push-Pull. The values of the grid condensers & leak are arranged to give squeezing. Since the frequency of the squeeze is variable the whole circuit is biased into cut-off.

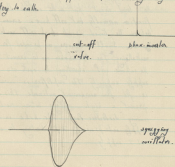
by the backing-off battery. The cut-off valve supplies a sharp impulse which is filtered by an amp-to-osc. This, now positive, pulse affects the bias of the circuit squeeze. The natural f of the circuit must be higher than f of the B.O. in order that the squeeze will stop before a second pulse from the B.O. arrives. R_1 is to prevent the cut-off valve impulse shooting through the battery to earth.




to pass R.F. work the pentode is unsuitable for reason of its high R_a . The triode is liable to internal feedback by virtue of C_{ga} & so will oscillate.

The triode is "screened" by a difference of potential between grid & cathode & if now the grid is earthed & the tuned circuit put on the cathode the valve will function normally but will have a screen, earthed, between the tuned circuit which will neutralise


C_{gc} . Small condensers are provided for external neutralising. The $\frac{1}{2}$ chokes are to prevent R.F. from the cathode coil shunting to earth via the H.T. supply capacity. The amplifier is "current fed" i.e. fed from near anode cutinode. This is to prevent a high voltage between the two lines causing dielectric loss. The choke in the H.T. supply is to prevent R.F. shunting to earth in H.T. supply.

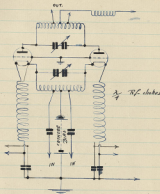


EXPT. 10.

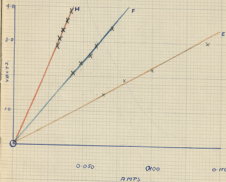


EXPT. 1 D.

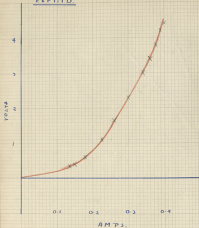


EXPT. 1 E.



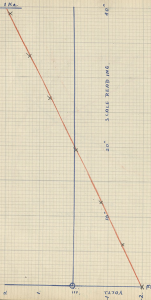






EXPT. 1A.

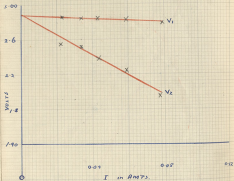


EXPT. 2A

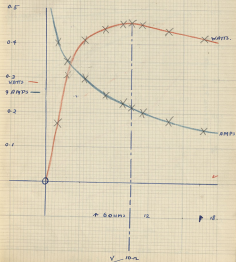

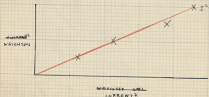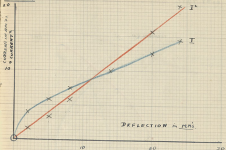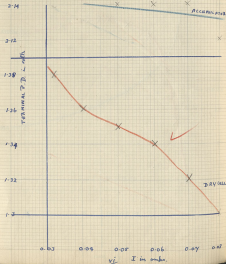

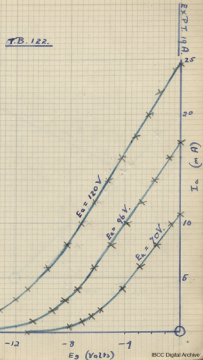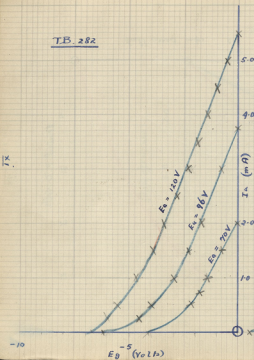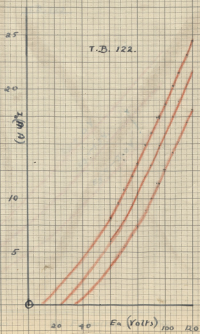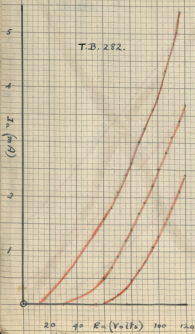

EXPT. 21

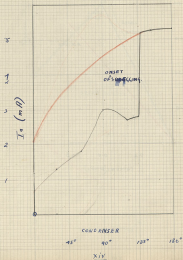

EXPT. 22

30 mV

2

1

0

-1

-2

-3

-4

-5

-6

-7

-8

-9

-10

-11

-12

-13

-14

-15

-16

-17

-18

-19

-20

-21

-22

-23

-24

-25

-26

-27

-28

-29

-30

20 mV (DC and AC only)

10 mV (DC and AC only)

5 mV (DC and AC only)

2.5 mV (DC and AC only)

1.25 mV (DC and AC only)

0.625 mV (DC and AC only)

0.3125 mV (DC and AC only)

0.15625 mV (DC and AC only)

0.078125 mV (DC and AC only)

0.0390625 mV (DC and AC only)

0.01953125 mV (DC and AC only)

D.C. volts or mV

